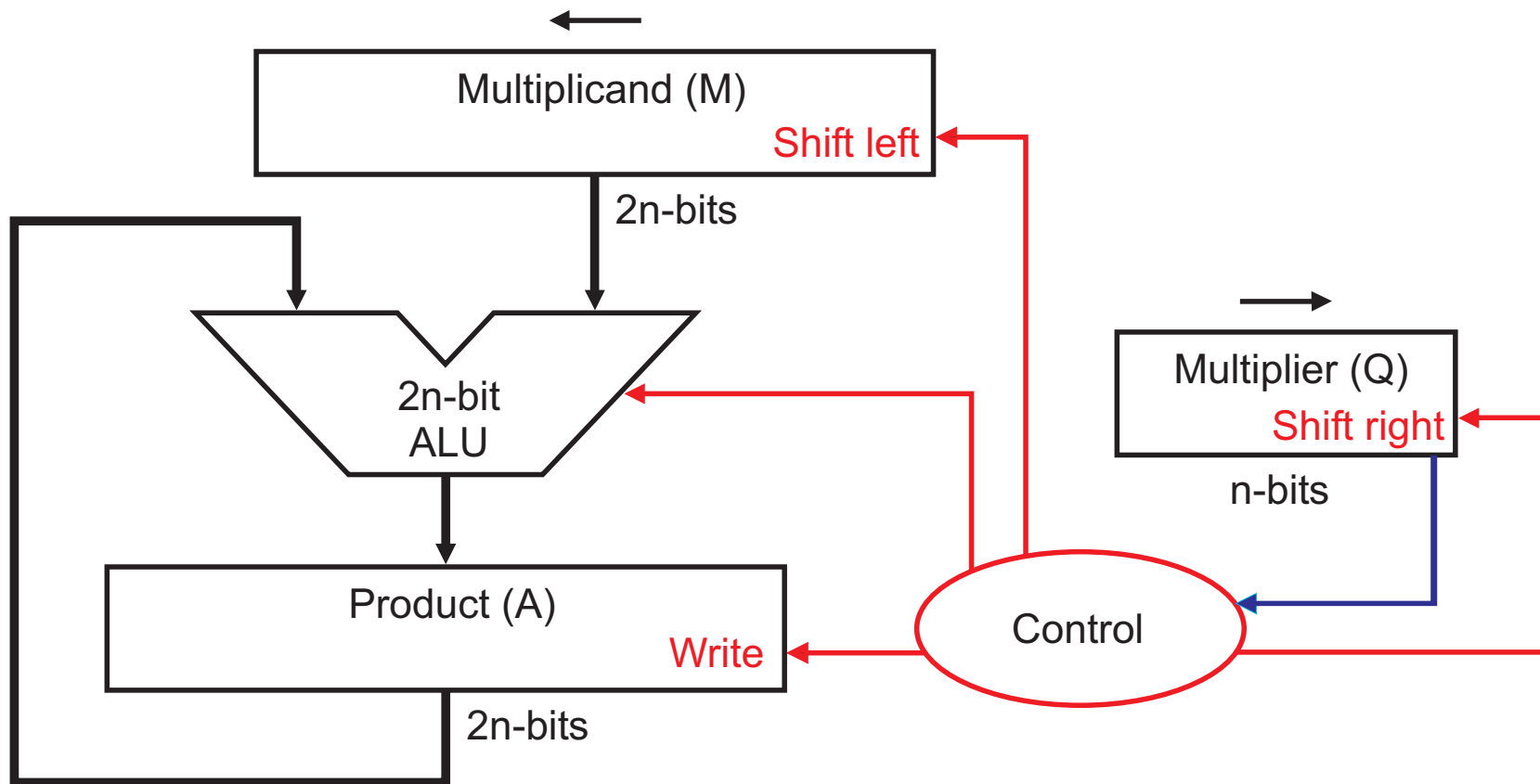



1011	M	(Multiplicand)	11
1101	Q	(Multiplier)	13
1011			
0000			
1011			
1011	+		
10001111	A	(Product)	143

Binary Integer Multiplication (unsigned)




$$M * Q = A$$


Multiplication Hardware (ver.1)

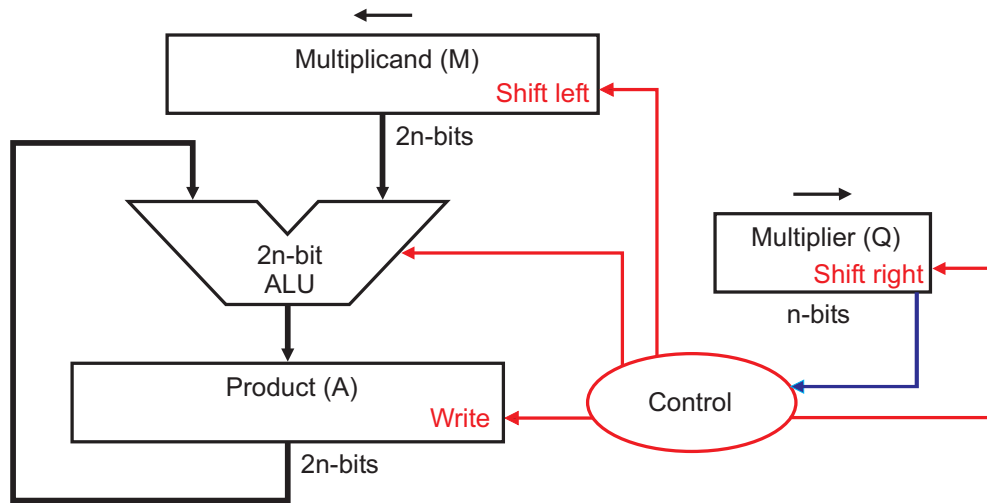

$$M * Q = A$$

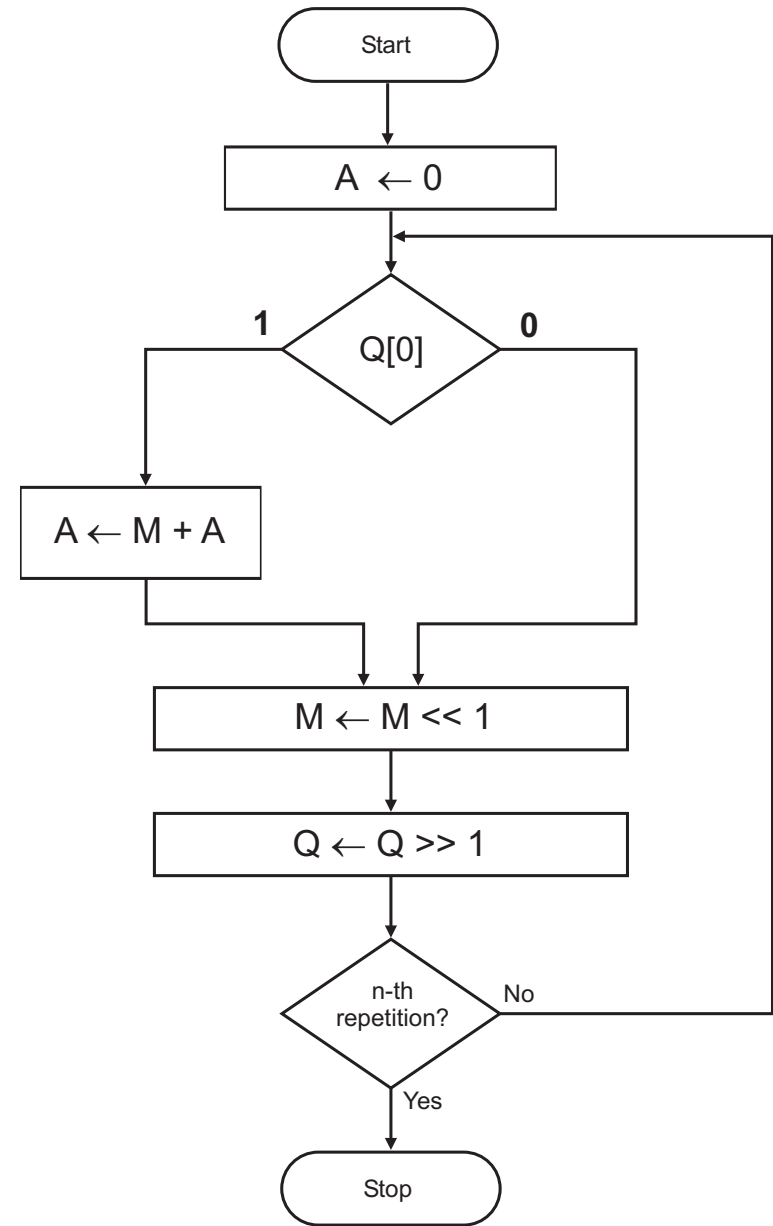


Multiplication Algorithm (ver.1)

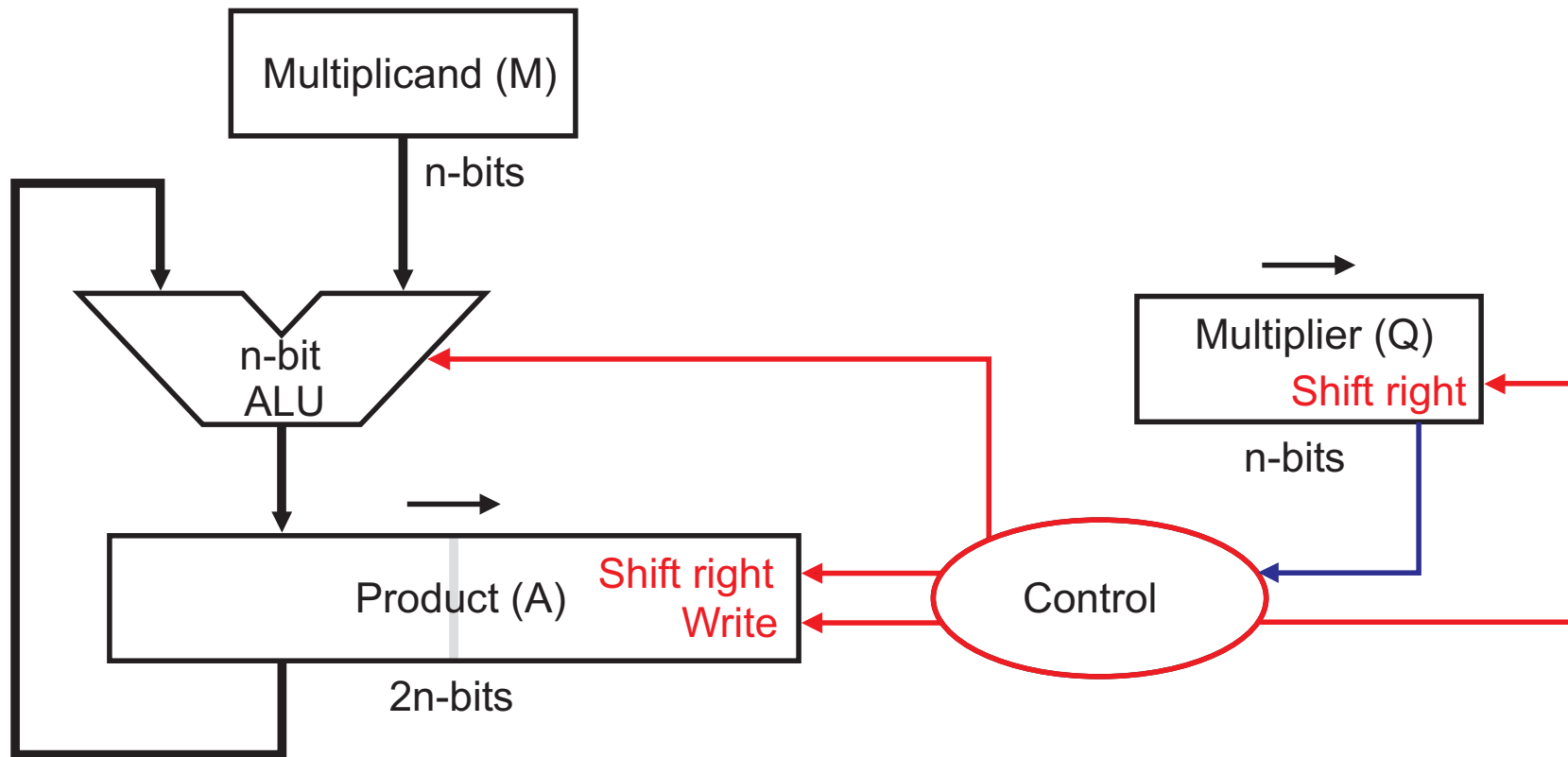


$$M * Q = A$$


Multiplication Hardware (ver.2)

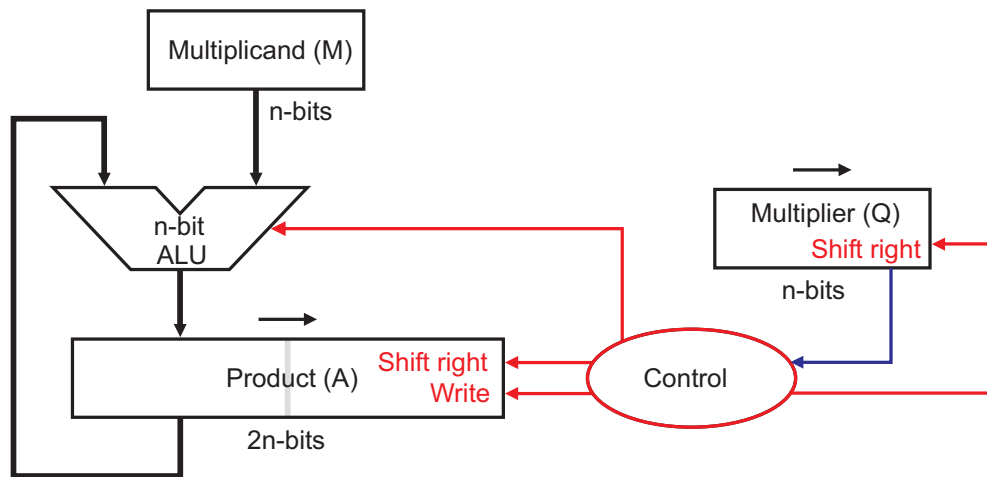

$$M * Q = A$$

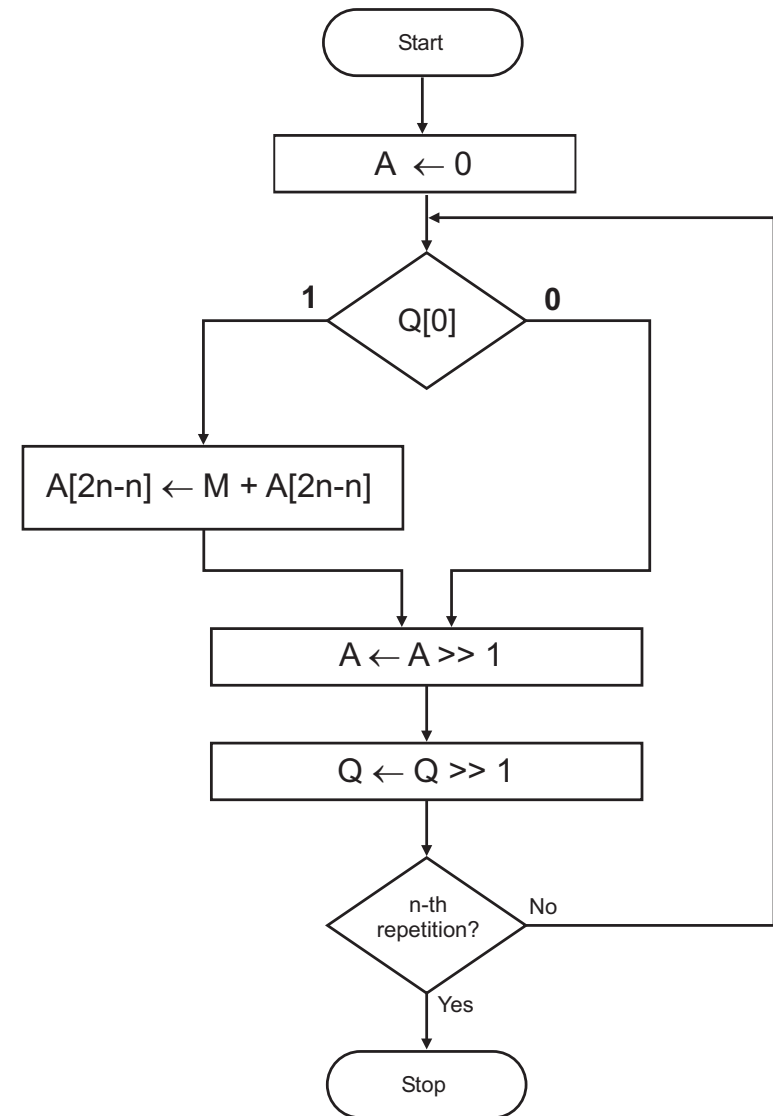


Multiplication Algorithm (ver.2)

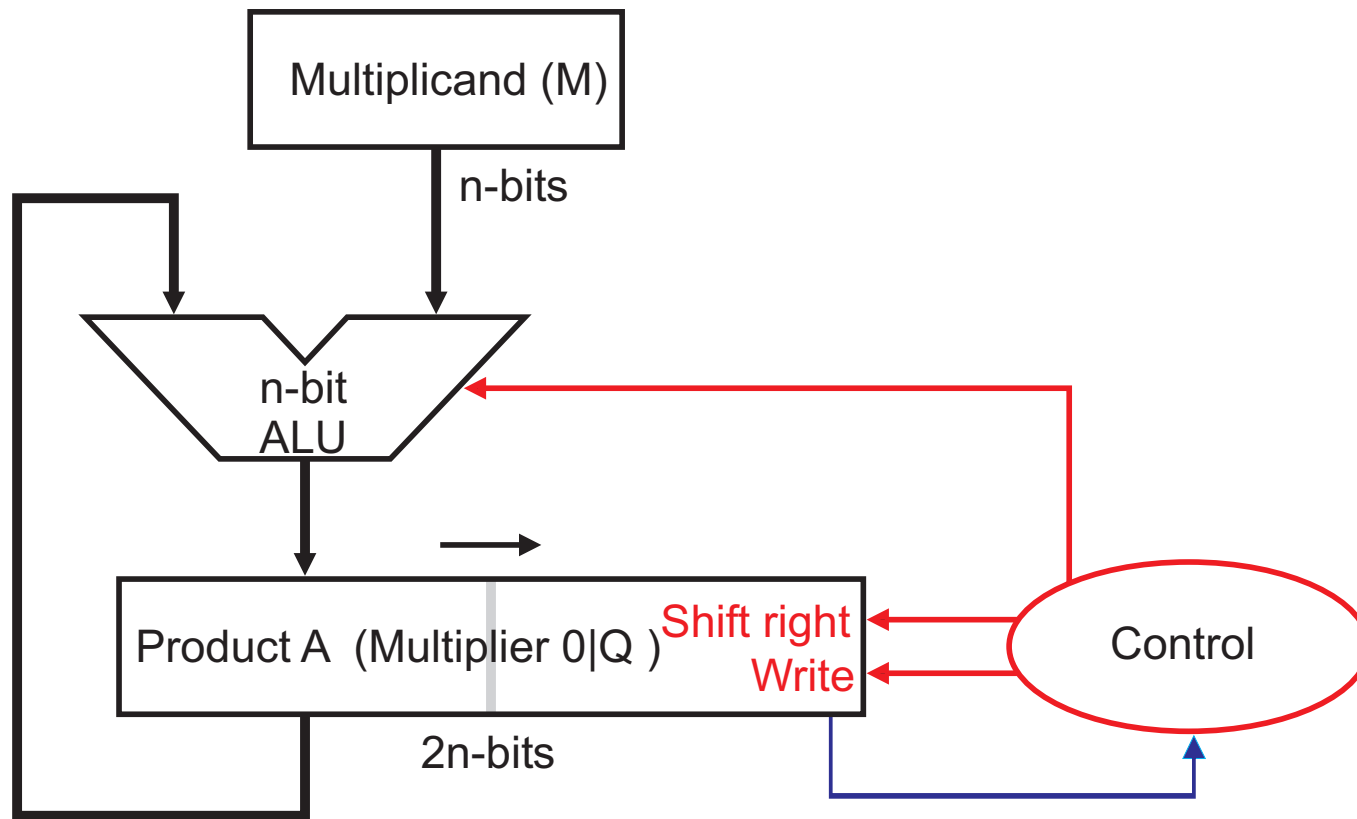


$$M * Q = A$$

Multiplication Hardware (ver.3)

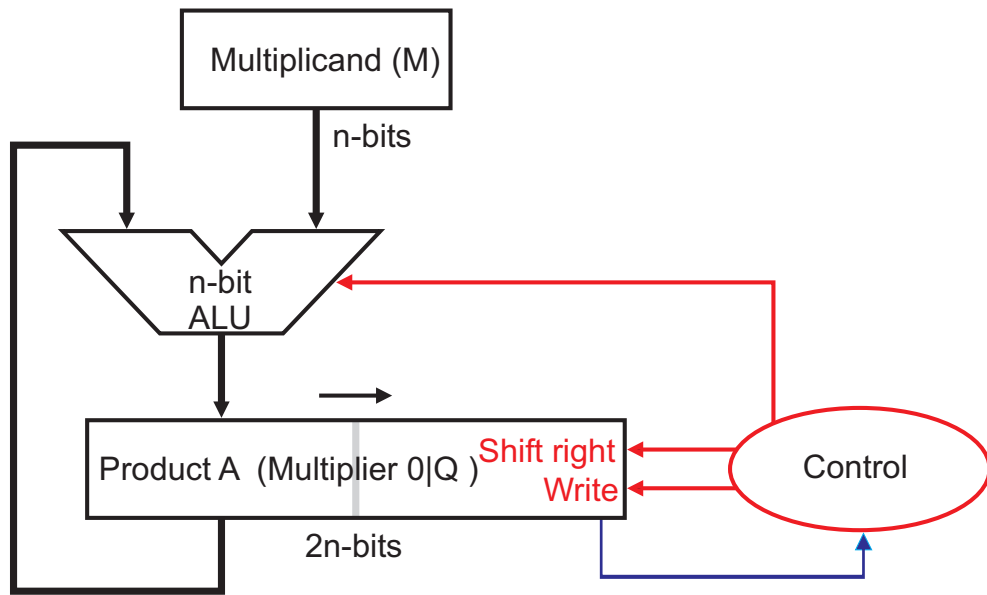



$$M * Q = A$$

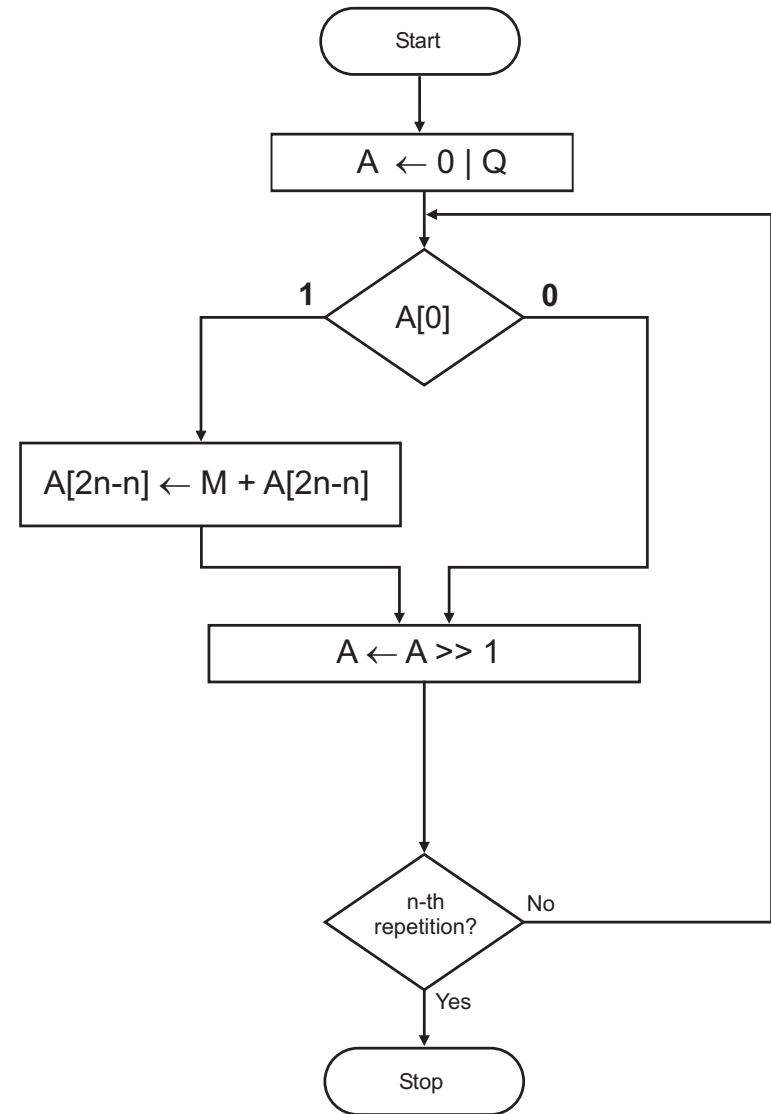

Multiplication Algorithm (ver.3)

	<u>1111 (15)</u>	<u>0011 (3)</u>	
+M	11110000		
>A	01111000		
+M	1 01101000		
>A	10110100		
>A	01011010		
>A	00101101	(45)	

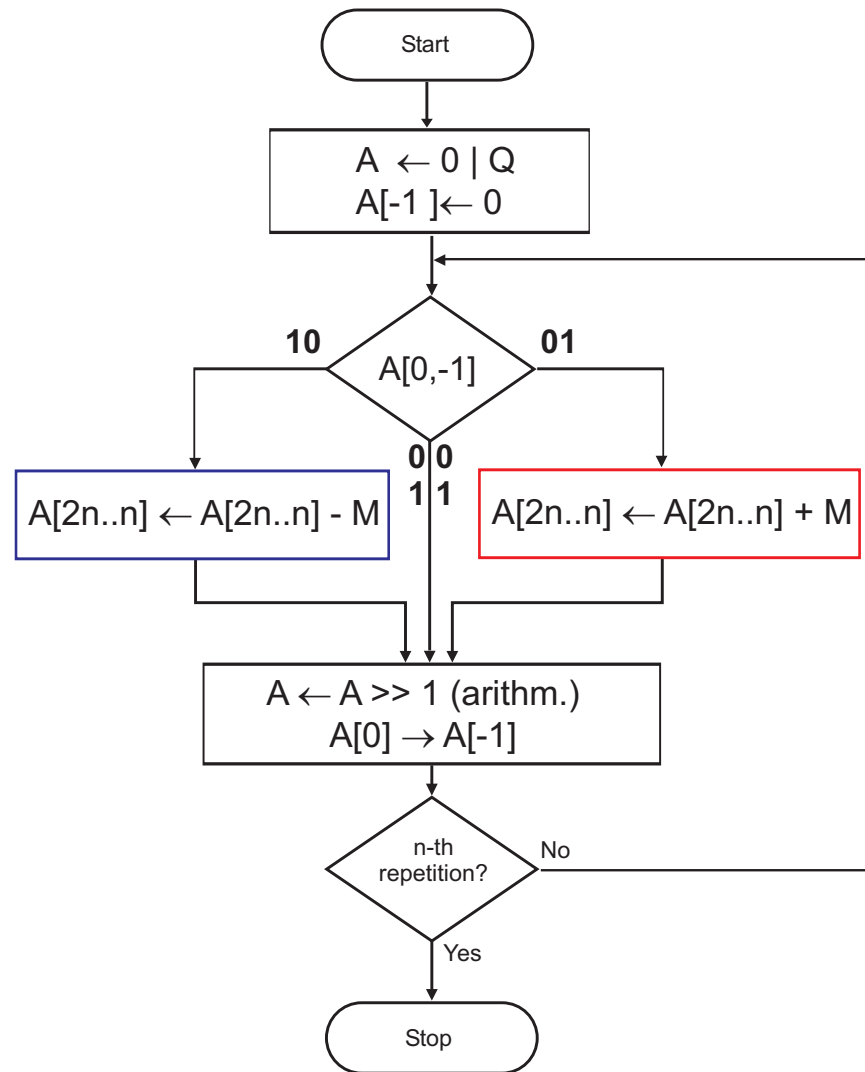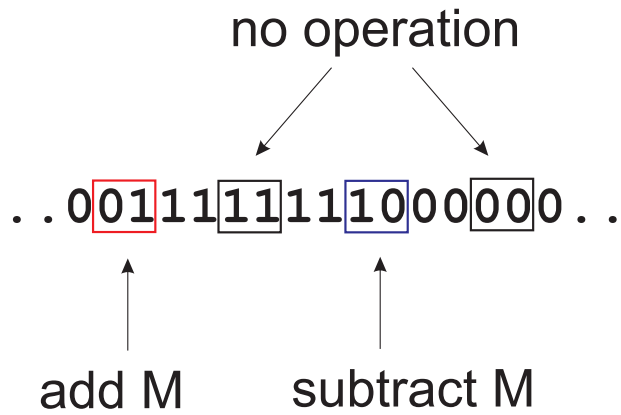Watch out for Carry Out during partial additions



Binary Integer Multiplication (signed) - Booth's Algorithm

$$Q = \overbrace{111 \dots 111}^{n-1 \dots k+1} \overbrace{0}^k \overbrace{a_{k-1} a_{k-2} \dots a_1 a_0}^{k-1 \dots 0} \quad (1)$$

$$Q = -2^{n-1} + \underbrace{2^{n-2} + \dots + 2^{k+1}}_{2^{n-1} - 2^{k+1}} + a_{k-1} 2^{k-1} + a_0 2^0 \quad (2)$$

$$Q = \underbrace{-2^{k+1}}_{\substack{\text{beginning} \\ \text{of the} \\ \text{last} \\ \text{all-ones} \\ \text{block}}} + \underbrace{a_{k-1} 2^{k-1} + \dots + a_0 2^0}_{\substack{\text{part guaranteed to be expressed} \\ \text{by additions and subtractions}}} \quad (3)$$


Representation of negative multiplier Q (2's C)
by additions and subtractions for all-ones blocks

Divisor = 1011	00001101 = Quotient (13)
(11)	<u>10010011</u> = Dividend

-	<u>1011</u>
	001110
-	<u>1011</u>
	00001111


-	<u>1011</u>
	00000100 = Remainder (4)

Binary Integer Division (unsigned)

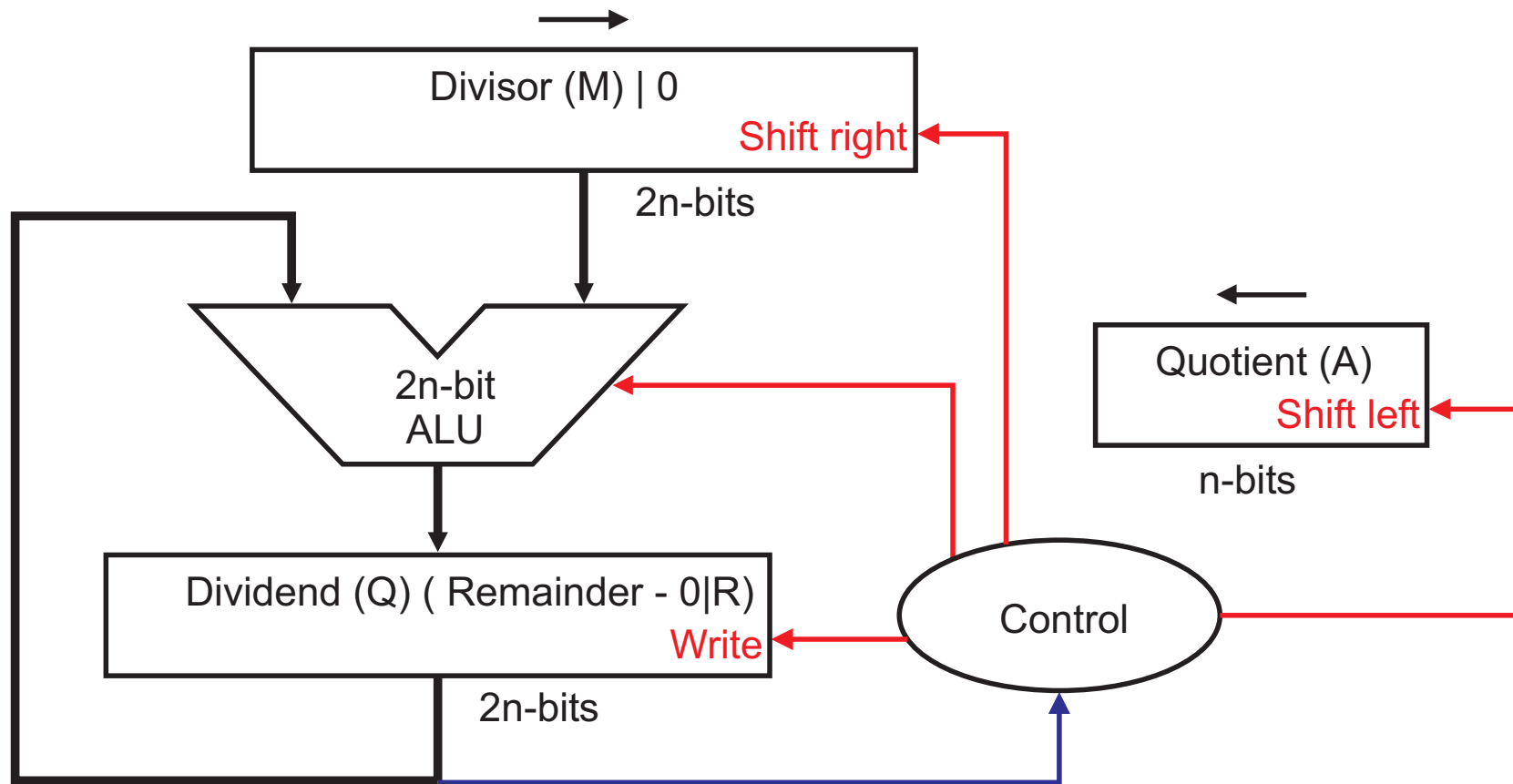


$$Q / M = A + R$$

Division Hardware (ver.1)

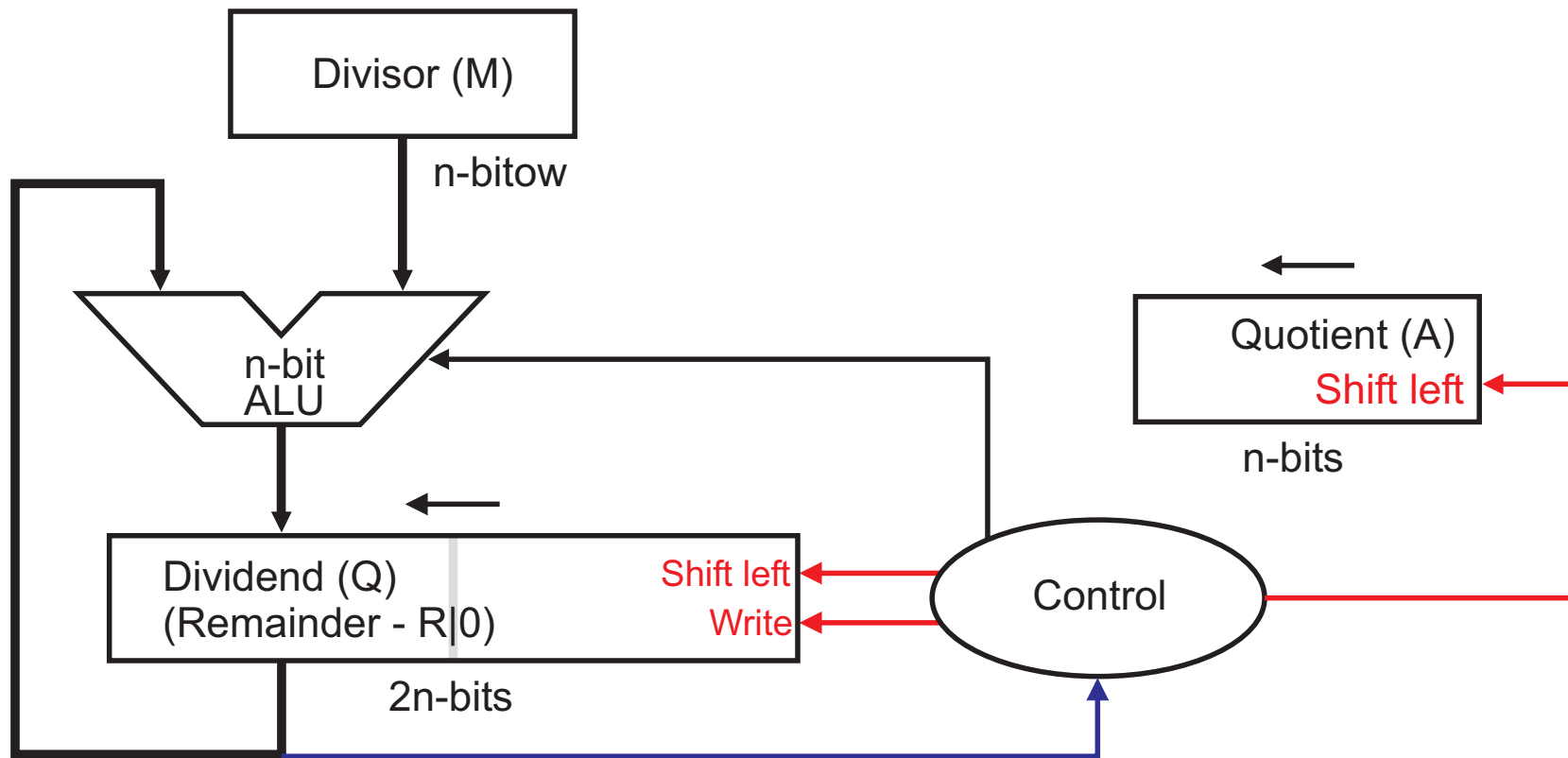


$$Q / M = A + R$$

Division Hardware (ver.2)

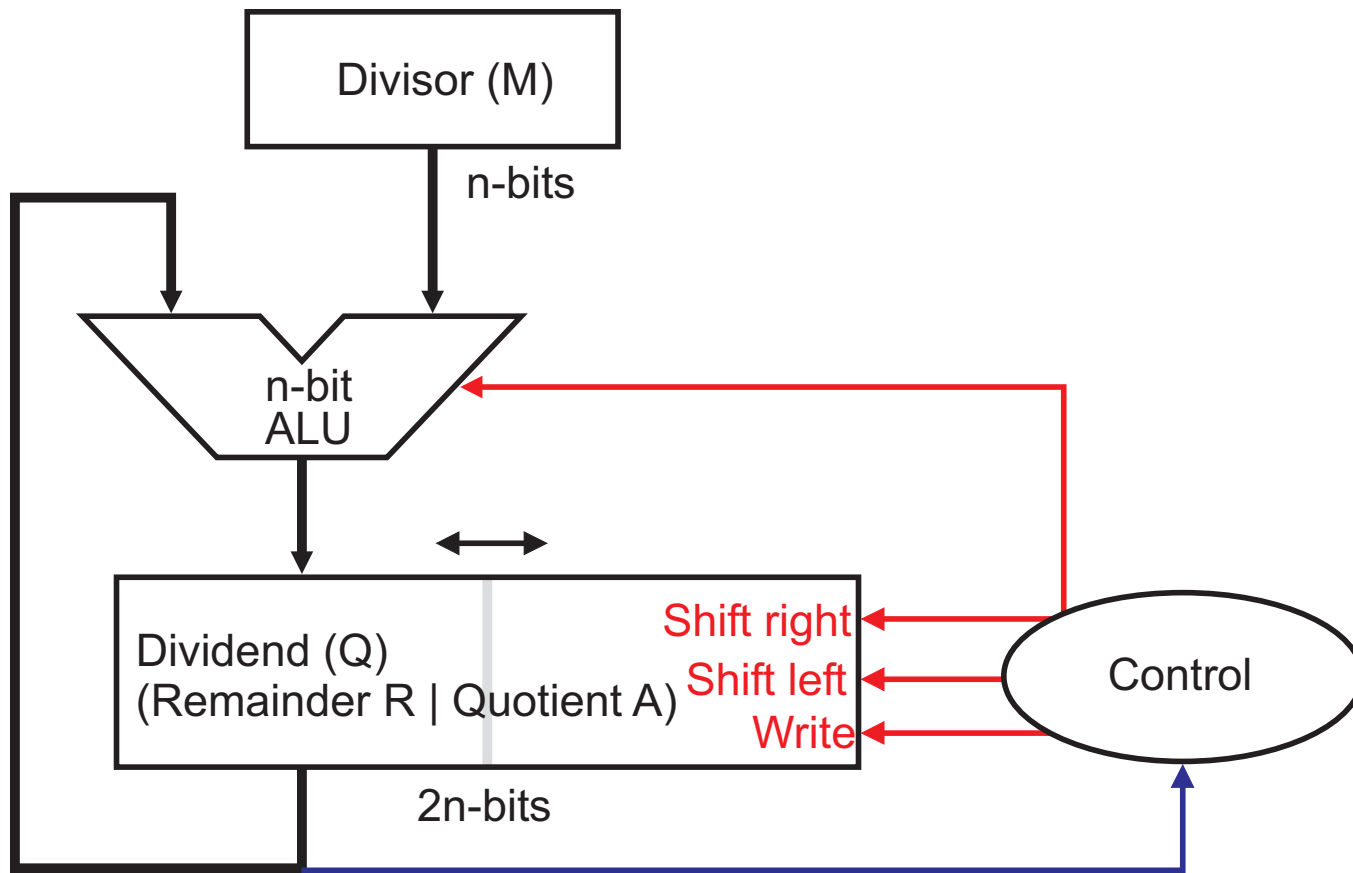


$$Q / M = A + R$$

Division Hardware (ver.3)

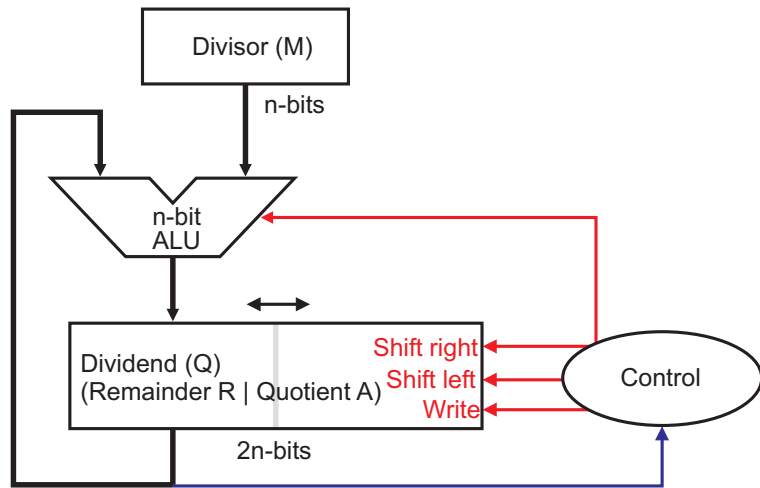

$$Q / M = A + R$$

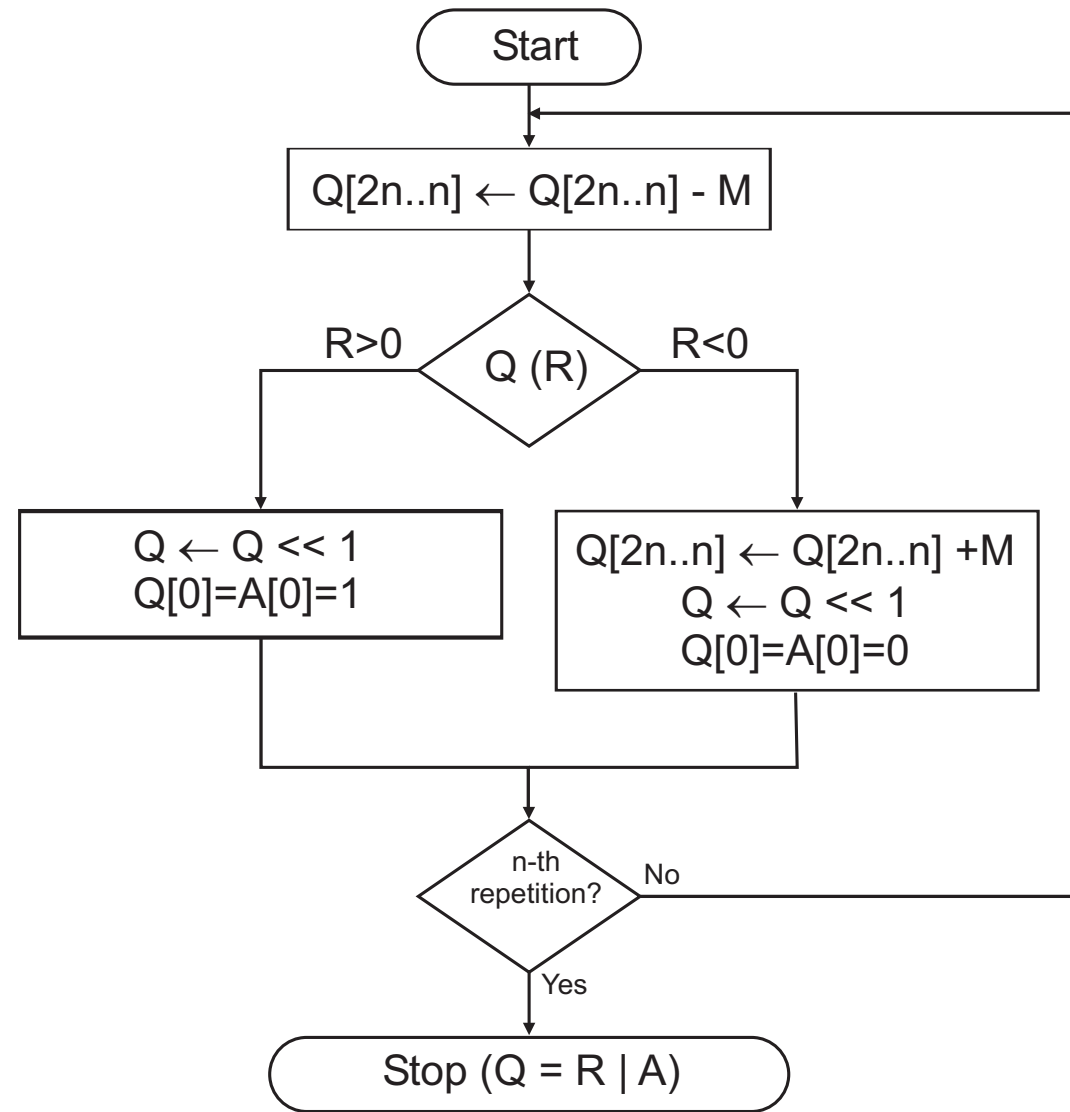

Division Algorithm (ver.3)