




Fast Multipliers

Fast Multiplication

- Additions and Multiplications are building blocks for complex function computation, digital signal processing, etc.
- A number of approaches possible:
 - Bit-serial – compact design, limited resources, relatively slowest, serial process may be an advantage
 - Multioperand addition – cost-effective implementations and high-performance arithmetic units
 - Divide & Conquer – decomposition of long multiplications into smaller tasks
 - Hybrid designs


Bit-Serial Processing

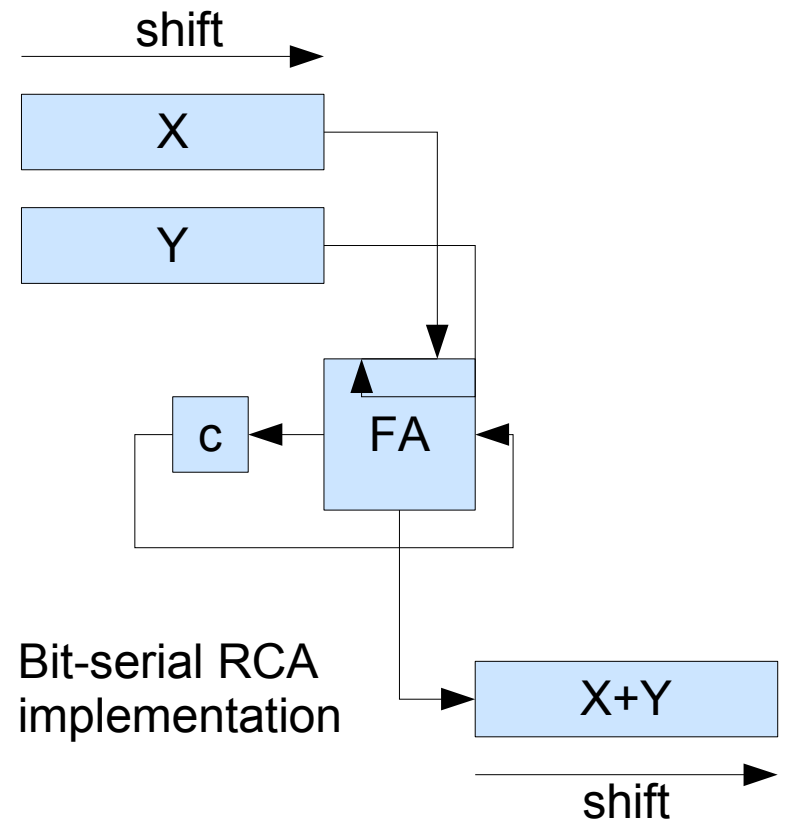- VLSI implementation advantages:
 - small pin count
 - reduced wire length
 - high clock rate
 - small space
 - low power consumption
- Alternative to pipeline units for parallel processing



Bit-Serial Multiplier

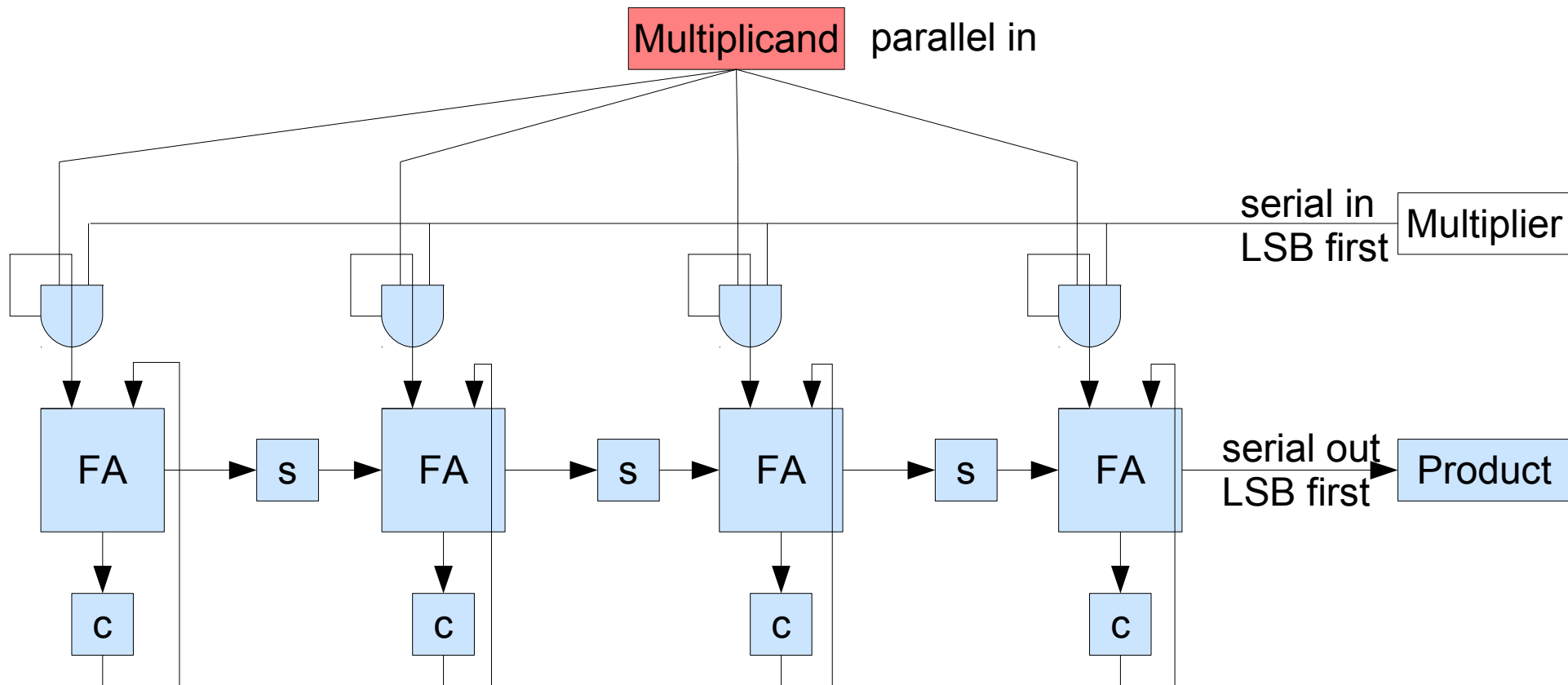- Semi- or fully-serial solutions exists
 - e.g. semi-serial 4×4
 - 2k cycles needed for $k \times k$ -bit multiplication



Multioperand Problem


Multiplication as multioperand addition

- Possible improvements:
 - add the operands faster →
tree & array multipliers
(various CSA configurations)
 - reduce the number of operands →
high-radix multipliers
operation on shorter operands

Basic Multiplication

- Add/Shift algorithm of k-digit numbers, $\Theta(k \log k)$

 A – Multiplicand, X – Multiplier, P – product



radix-2 digit [0,1]

↓


$$P^{i+1} = P^i + x_i * A * 2^i$$

↑


shift i-positions

- In radix-2, multiple (the term $x_i * A$) is either 0 or A, thus simple
- Unnecessary demand of resources (long adder)

Shift Right(Left) Approach

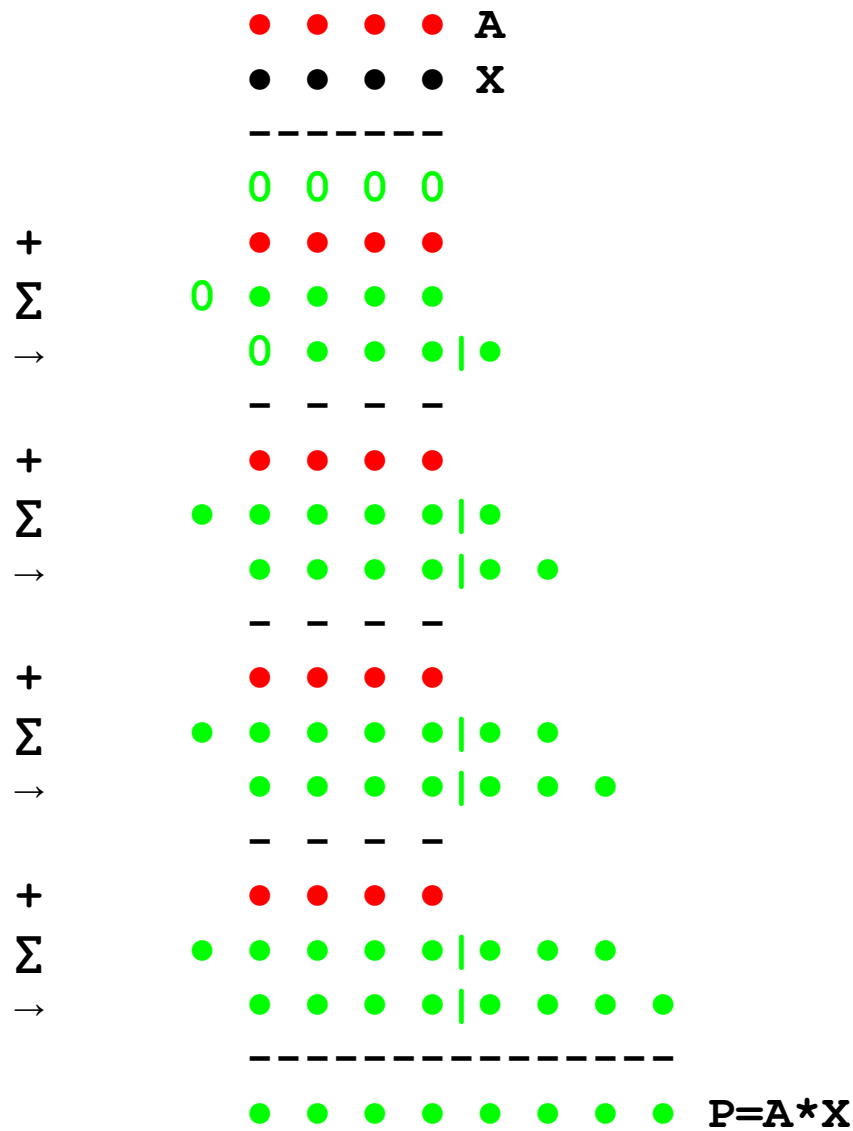

 
$$P^{i+1} = (P_{\text{(upper)}}^i + x_i * A) * 2^{-1}$$



$$P^{i+1} = 2^1 * P^i + x_{k-i-1} * A$$

Realizations

Hardware Shift Right

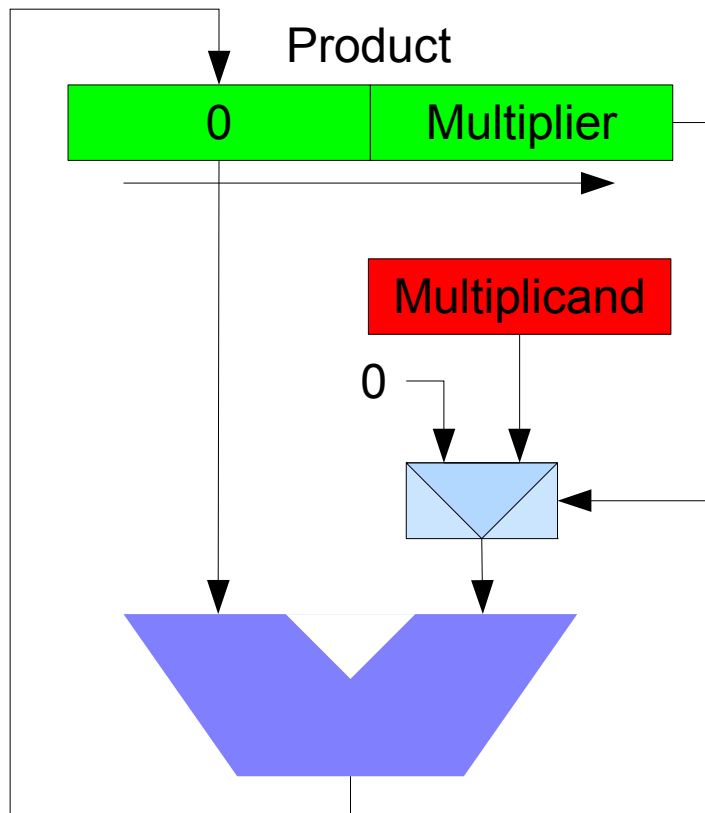

Software Shift Left

```
* initialize
  move.w  #A, RA
  move.w  #X, RX
  move.l  #0, RP
  move.b  #k, RC



* start
next  lsl.l  #1, RP
      lsl.w  #1, RX
      bcc   skip
      add.l  RA, RP
skip  sub.b  #1, RC
      bne   next

* done
```

Motorola 68000 Assembler

Radix-4 Multiplication

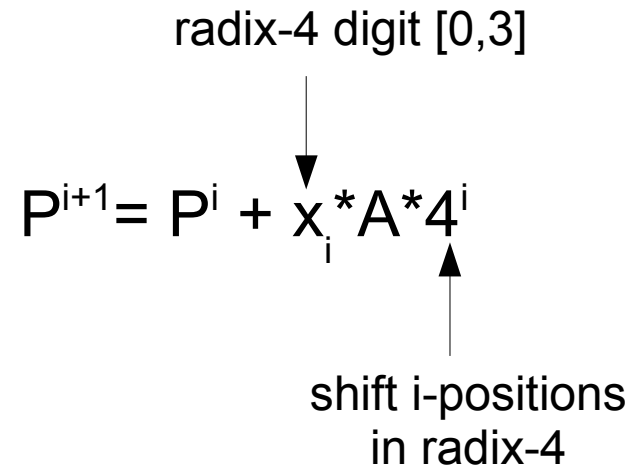 
- k-digit radix-2 number = $\frac{1}{2}k$ -digit radix-4 number
- Require multiples: 0, A, 2A, 3A, thus not so simple



- 0, A, 2A can be provided easily (2A by shifting)
- 3A (yet another addition ?)

Precomputation of Multiples

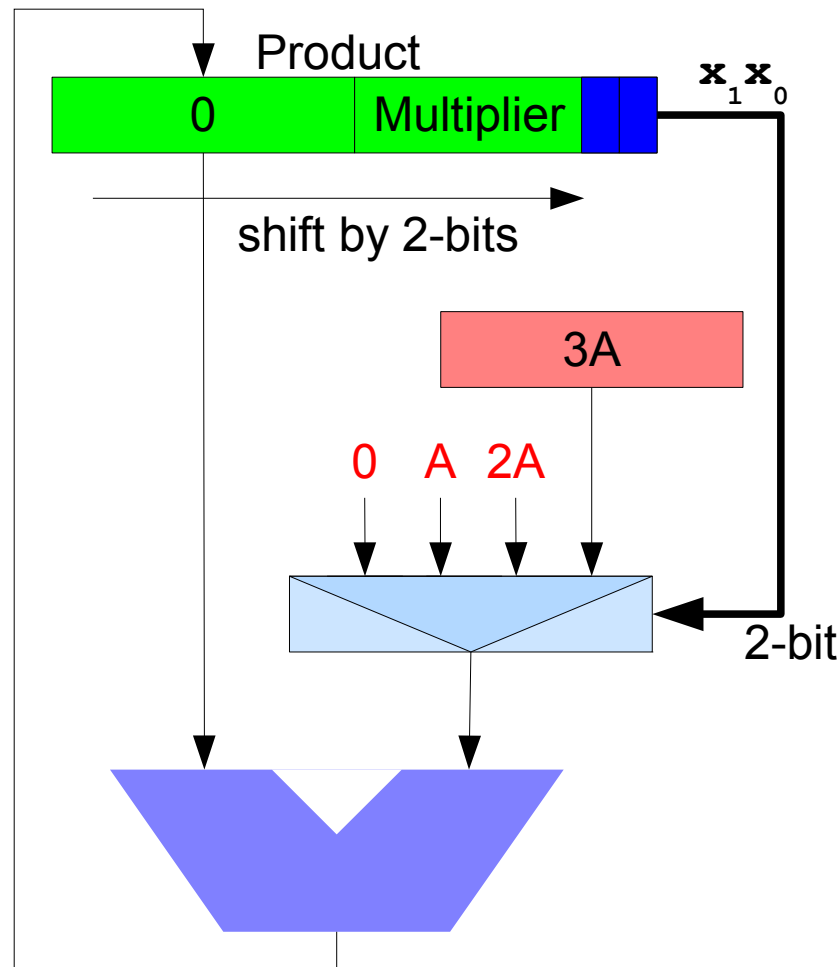
- Compute $3A$ once and use many times later
- Solution does not scale well to radix-8, radix-16,...



Radix-4 Multiplier

Computing Multiples with CSA

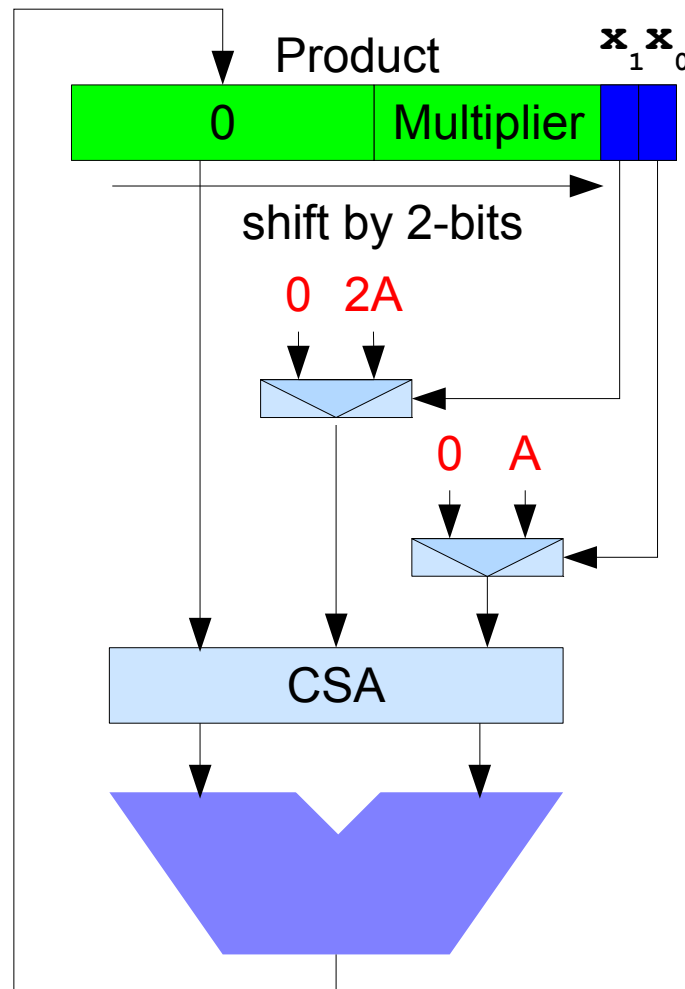- CSA's offer a solution to fast computation of $3A$ (and other in higher radices) multiples



Partial tree architecture

CSA's introduce a delay in each step of multiplication. In higher radices this delay can be significant.

Radix-4 Multiplier


Multiples Generation with Carry

Multiples can be handled as (in radix-4):

3A = Carry - A

4A = Carry

x1	x0	cin	Multiple	cout
0	0	0	0	0
0	0	1	A	0
0	1	0	A	0
0	1	1	2A	0
1	0	0	2A	0
1	0	1	-A	1
1	1	0	-A	1
1	1	1	0	1

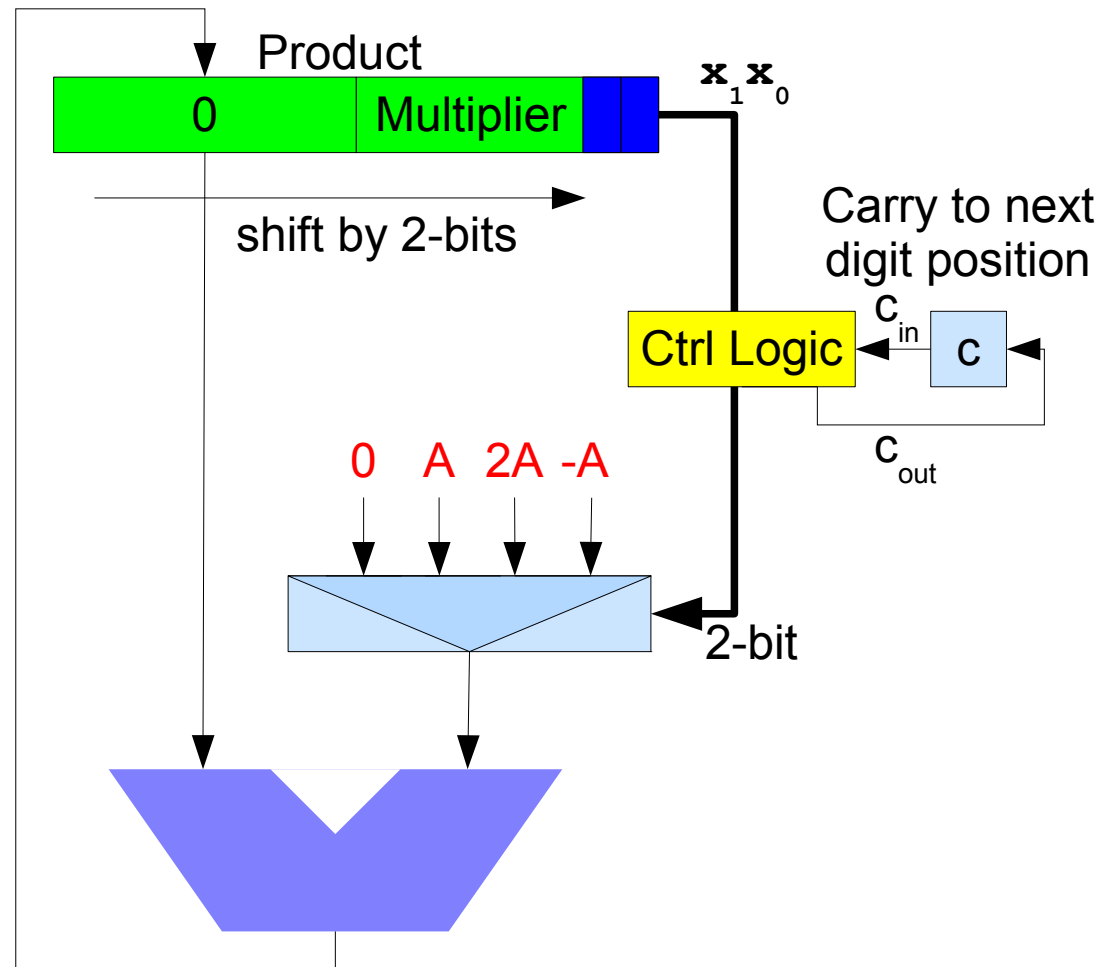

Radix-4 Multiplier

Multiples Generation – Example



Only 2-steps of algorithm in radix-4

	0101	→ 5 (A)	
	0111	→ 7	

	0000		
{	+	1011	(3A → -A & Carry generated)
	Σ	1011	
	→	001011	
	+	0101	+1 (1A + Carry)
	Σ	100011	
	→	00100011	


	00100011	→ 35	

Multiples Generation with Carry

Method scales to radix-8 (precomputation needed), but is not practical for higher radices

radix-8: $3A$ must be precomputed

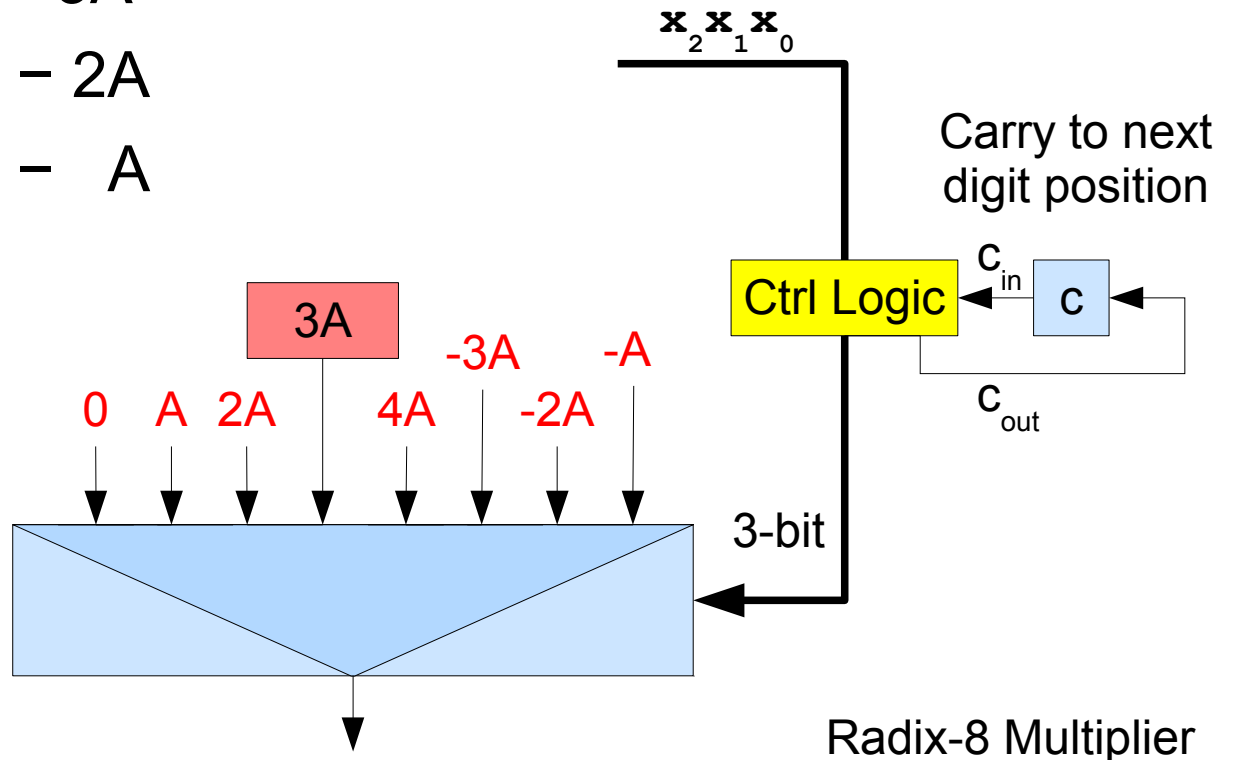- $5A \rightarrow \text{Carry} - 3A$
- $6A \rightarrow \text{Carry} - 2A$
- $7A \rightarrow \text{Carry} - A$
- $8A \rightarrow \text{Carry}$



Booth's Recoding – Signed Arithmetics

- Any chain of ones (1) in radix-2 numbers can be handled by just two operations: subtraction at the beginning and addition at the end of chain

$$\dots 00\underbrace{11\dots 11}_{j}00\dots = 2^j + 2^{j-1} + \dots + 2^{i+1} + 2^i = 2^{j+1} - 2^i$$

- Radix-2 operands can be converted (recoded) to BSD (redundant, radix-2, signed-digit system with set [-1, 1])


$$\dots 00\underbrace{11\dots 11}_{j}00\dots = \dots 0\underbrace{100\dots 0}_j \underbrace{-1}_{i} 00\dots$$

- Recoding properly handles negative (2's complement) numbers – signed multiplication possible

Radix-2 Recoding

NBC (radix-2, digit set $[0,1]$) \rightarrow BSD (radix-2, $[-1,1]$)

 
- 00 or 11 – inside chain of 0's or 1's – recode as 0
- 10 – beginning of 1's chain – recode as -1
- 01 – end of 1's chain – recode as 1



- Recoding is fast – no carry propagation
- Recoded i -digit depends directly on i -th and $i-1$ digits

Multiplication with Recoding

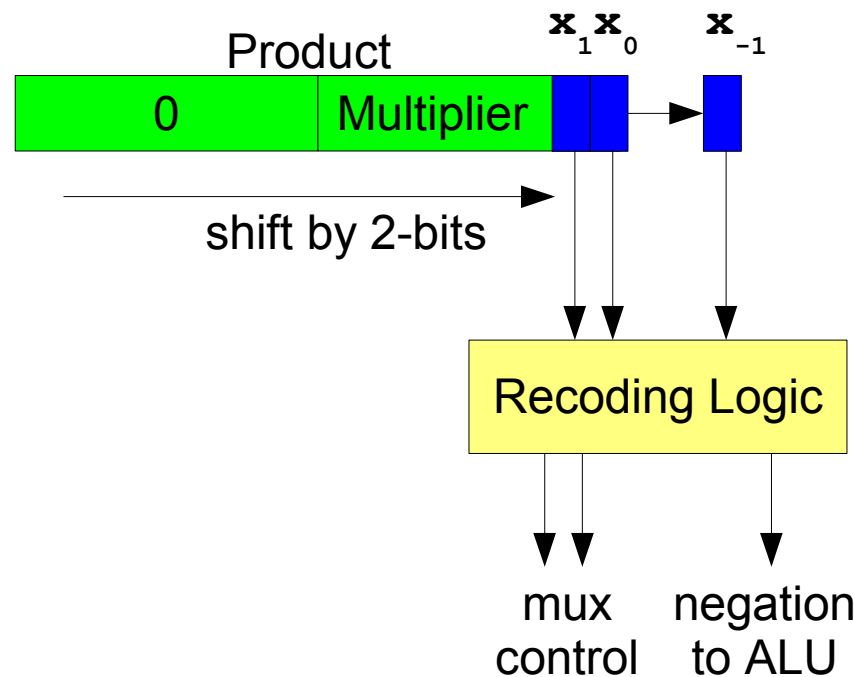- If multiplier is recoded (radix-4 $[-2,2]$), than possible multiples are: $0, \pm 1A, \pm 2A$, thus simple
- 3-bit of multiplier are needed for coding each radix-4 digit of multiplier




Booth's Algorithm

Radix-4 Multiplier


Radix-4 Multiplier – Signed Arithmetics

with Booth's Recoding

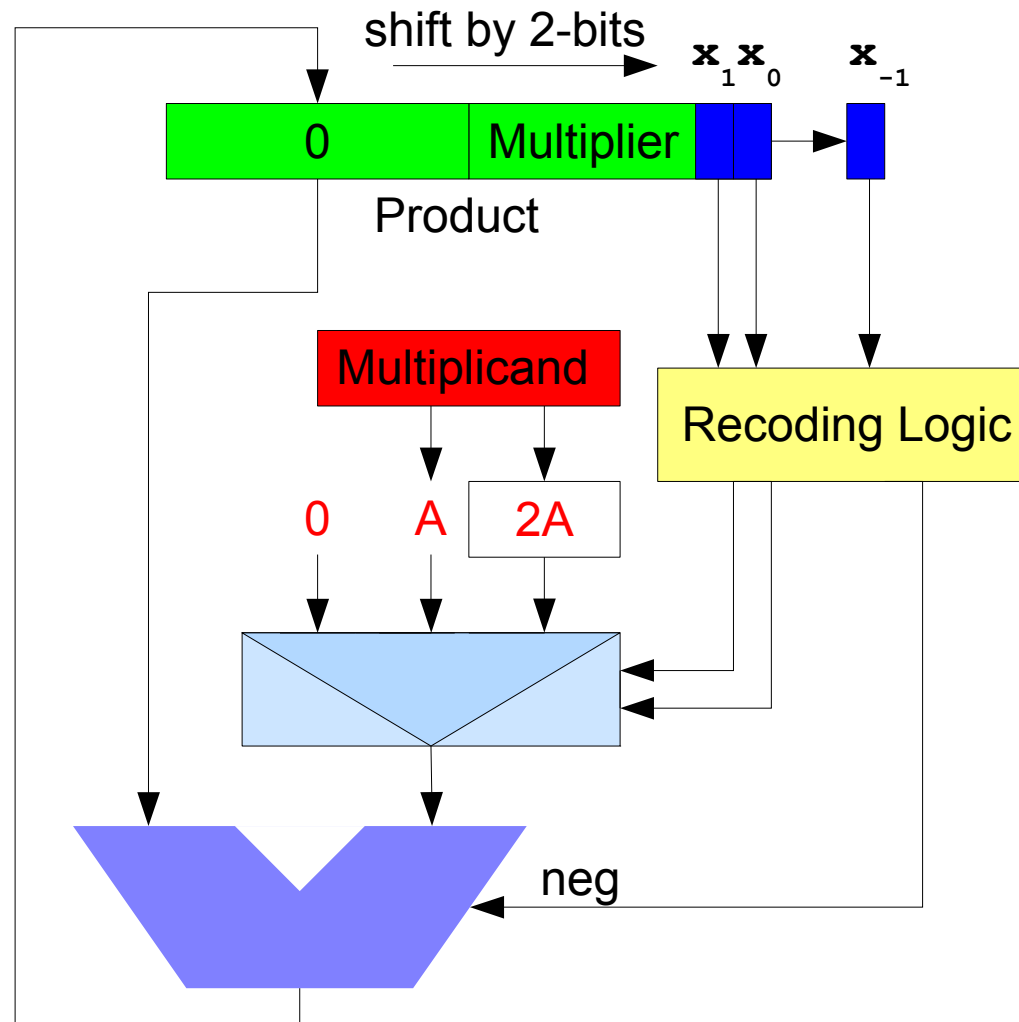


Improvement with CSA's

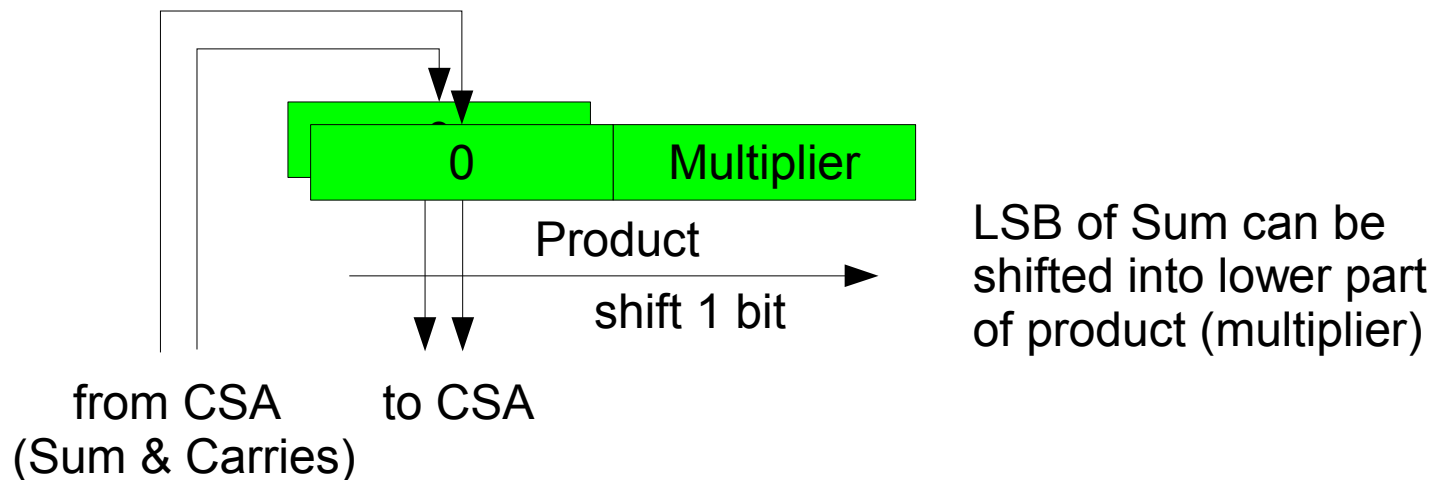- Partial additions can be done with CSA, thus significantly faster, $\Theta(k)$ instead of $\Theta(k \log k)$
- Upper part of product must be kept as redundant number, proper for CSA operation
- Final conversion will require CPA once, for the upper part of product only




Fast Radix-2 Multiplier

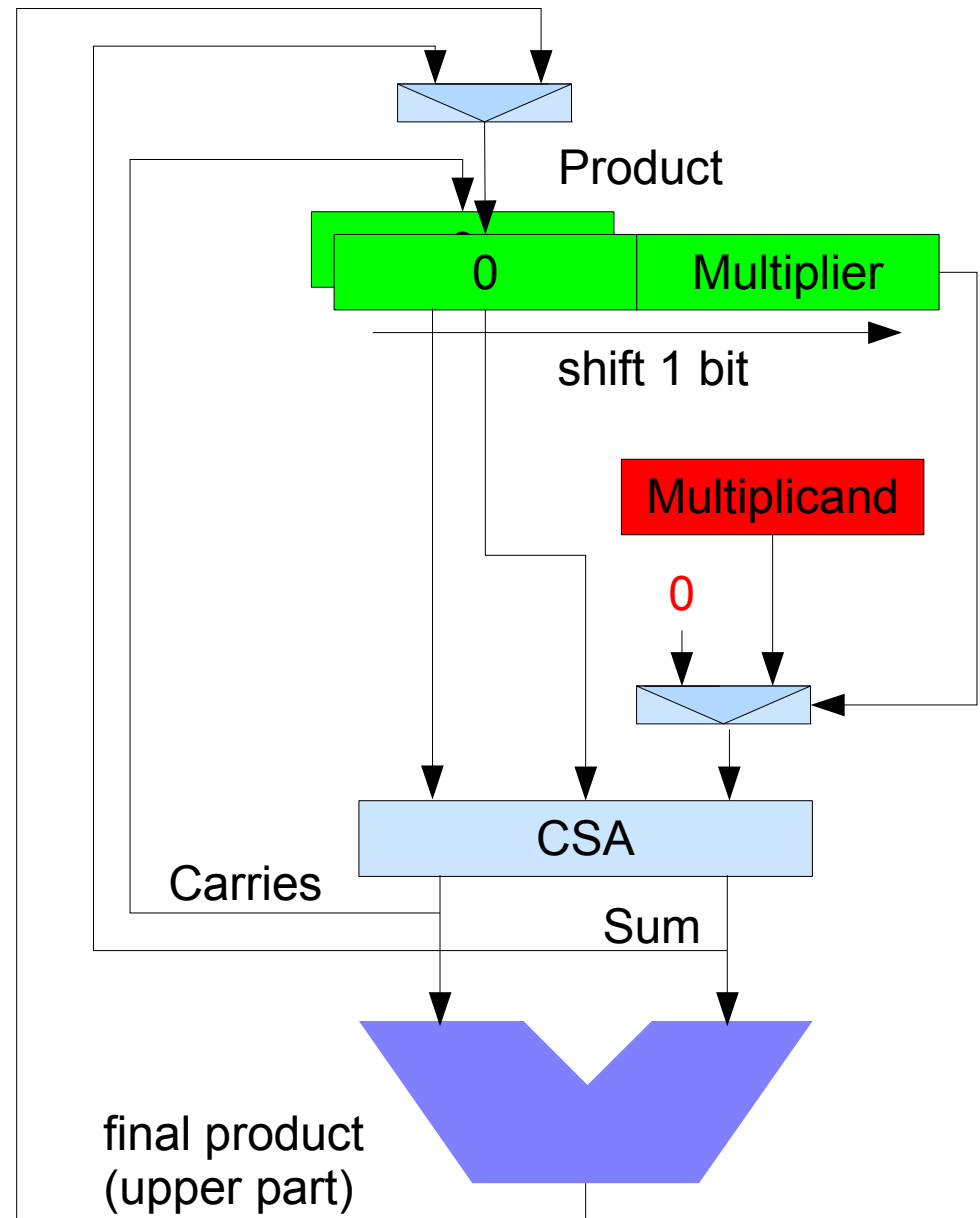- Few more resources compared to simple sequential architecture
- Latency $\Theta(k + \log k)$ instead of $\Theta(k \log k)$




Fast Radix-4 Multiplier

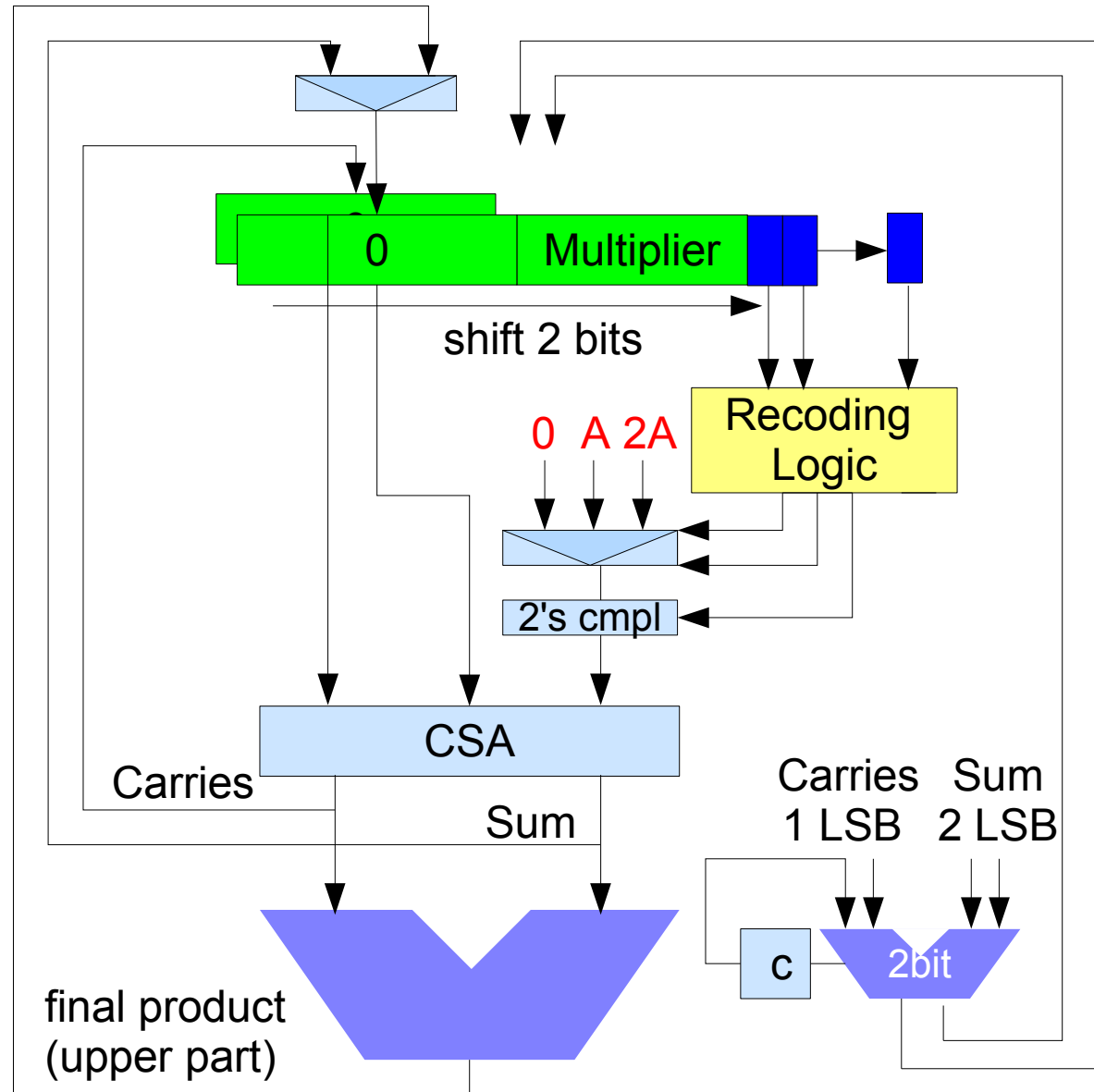- Latency $\Theta(k + \log k)$ but with radix-4 digits - fast
- Separate 2's compl. unit is needed
- Computation of shift-in 2-bits is required



Unsigned vs Signed Multiplication

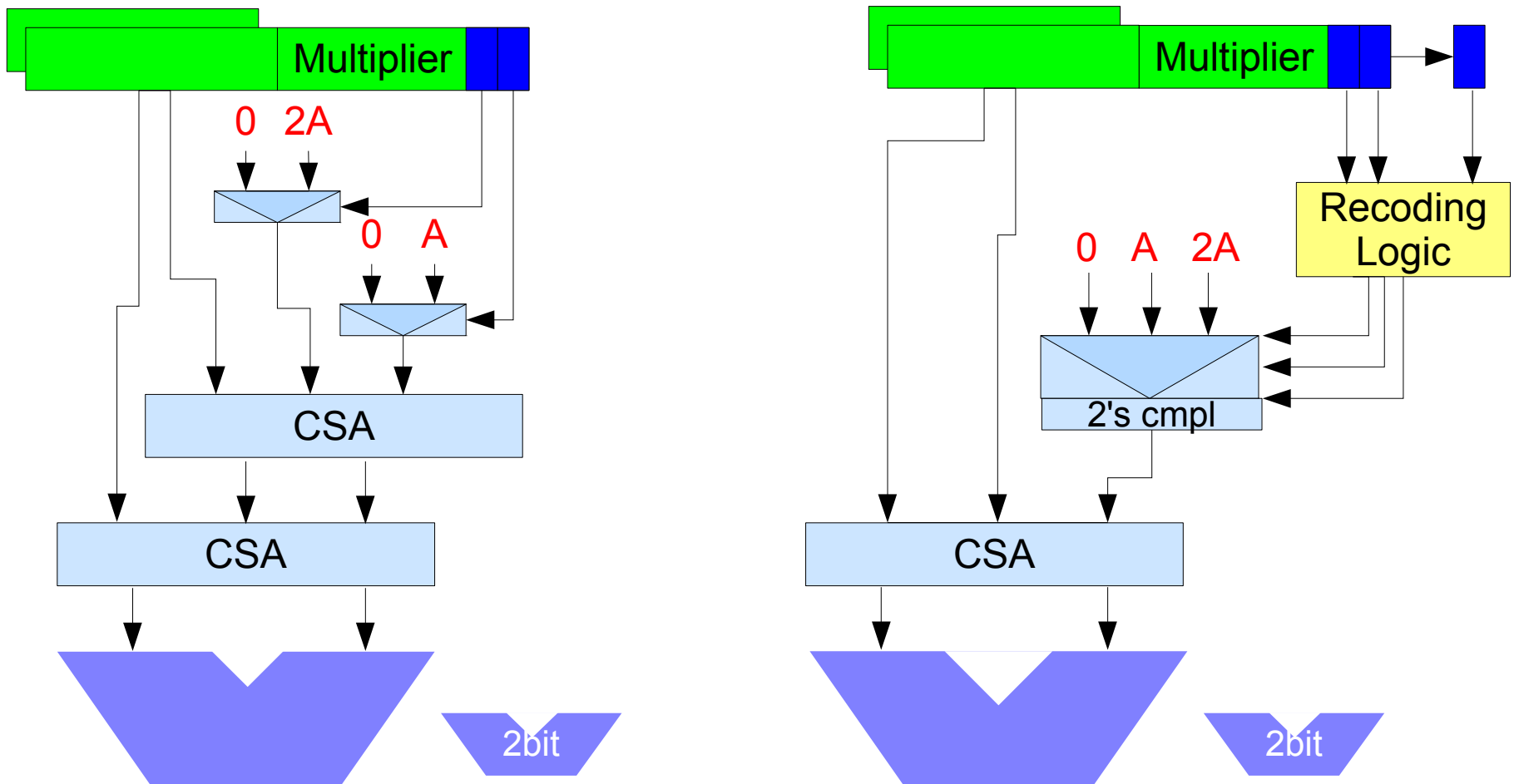
- Partial Tree and Recoding Architectures
- Both architectures scale well for higher radices



Radix-4 Multipliers


Radix-16 with Recoding – Example

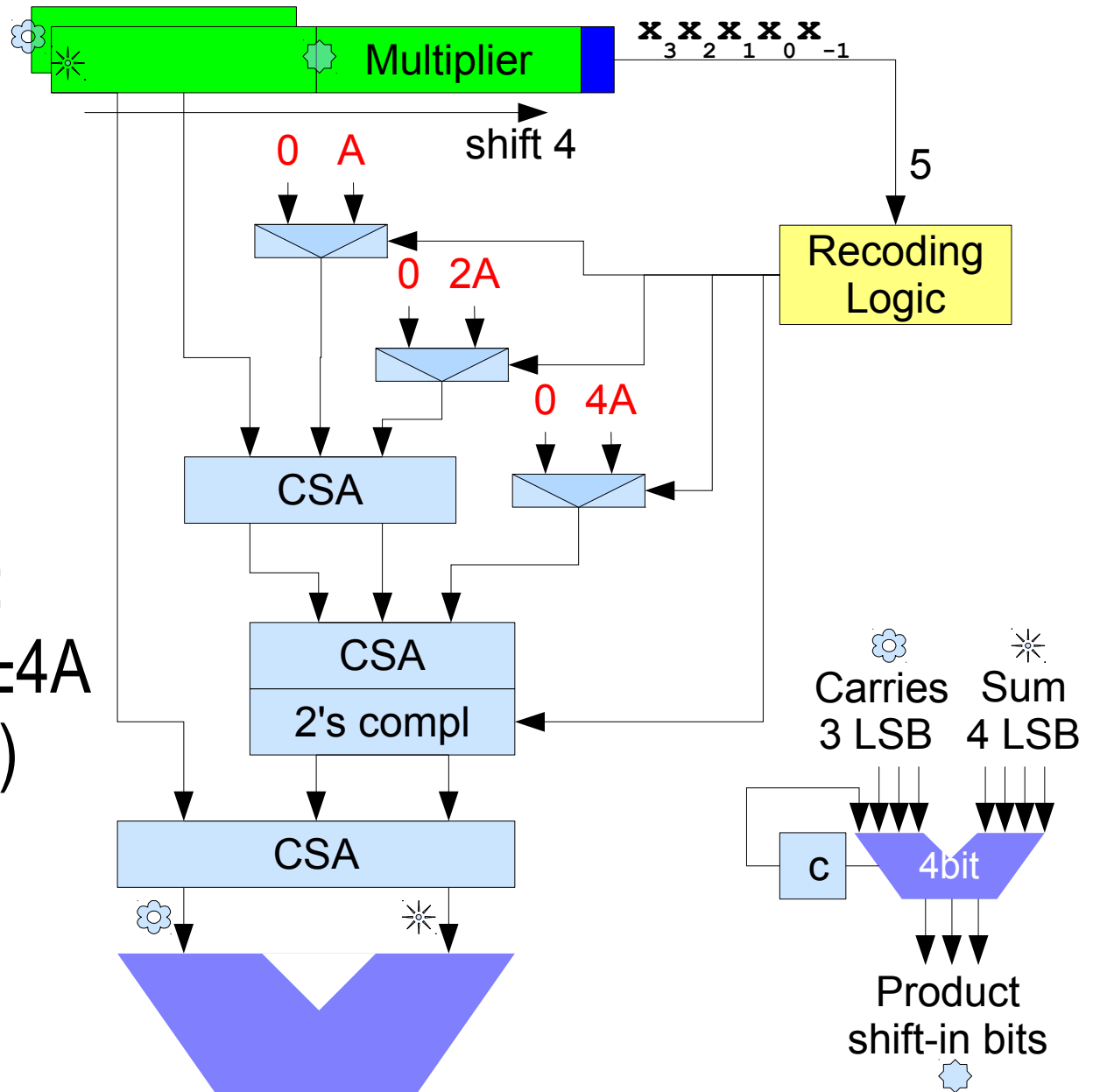- Shift by radix-16 digit (4 bits)
- Recoding use $[-4, 4]$ digit set (5 bit analysis)
- Multiples needed: $0, \pm 1A, \pm 2A, \pm 3A, \pm 4A$ (all with CSA tree)
- Signed arithmetic




Radix-16 with Partial Tree – Example

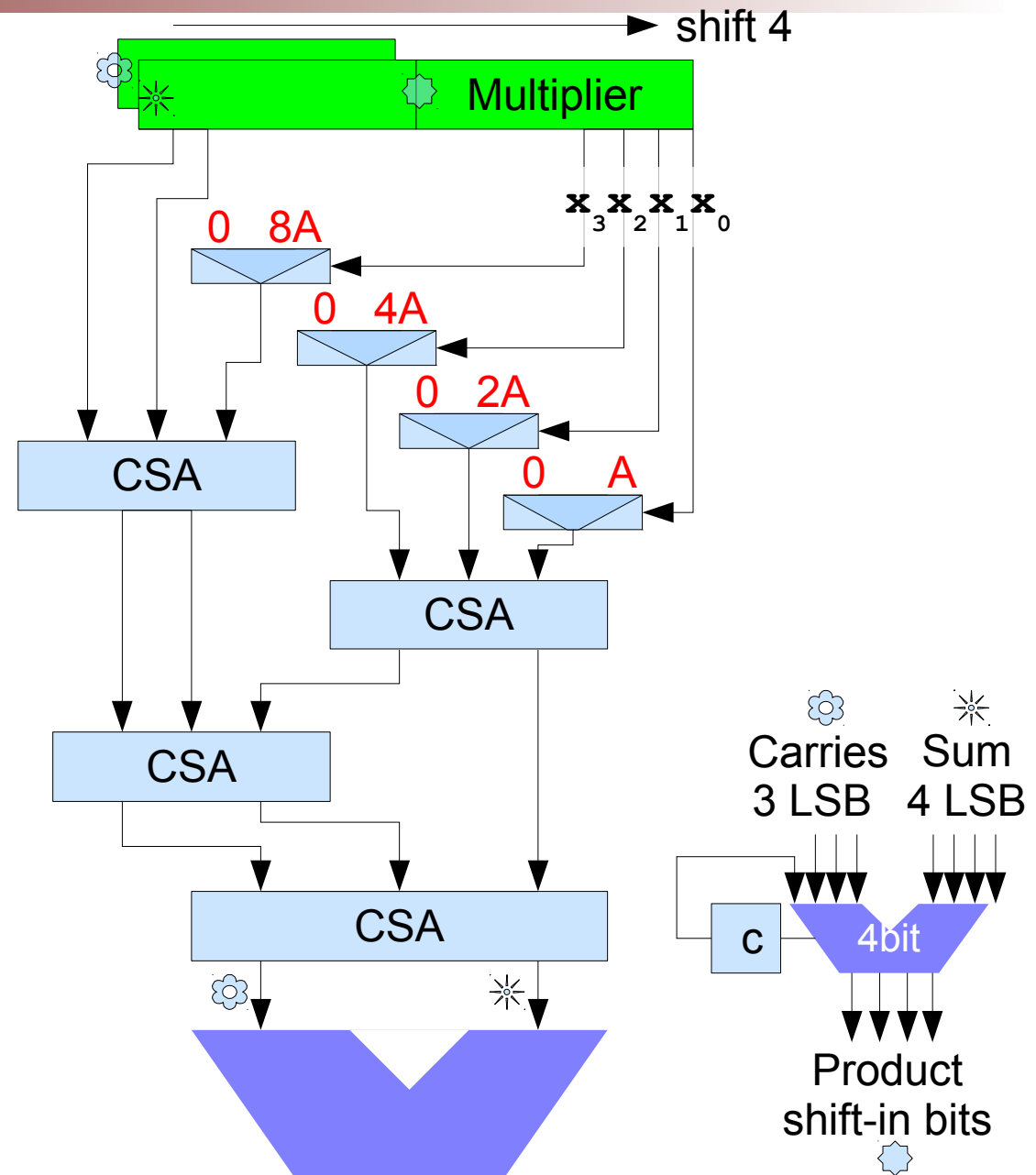- Shift by radix-16 digit (4 bits)
- Multiples 0 – 15A generated with 3-level CSA tree
- Unsigned arithmetic



Multipliers – Big Picture

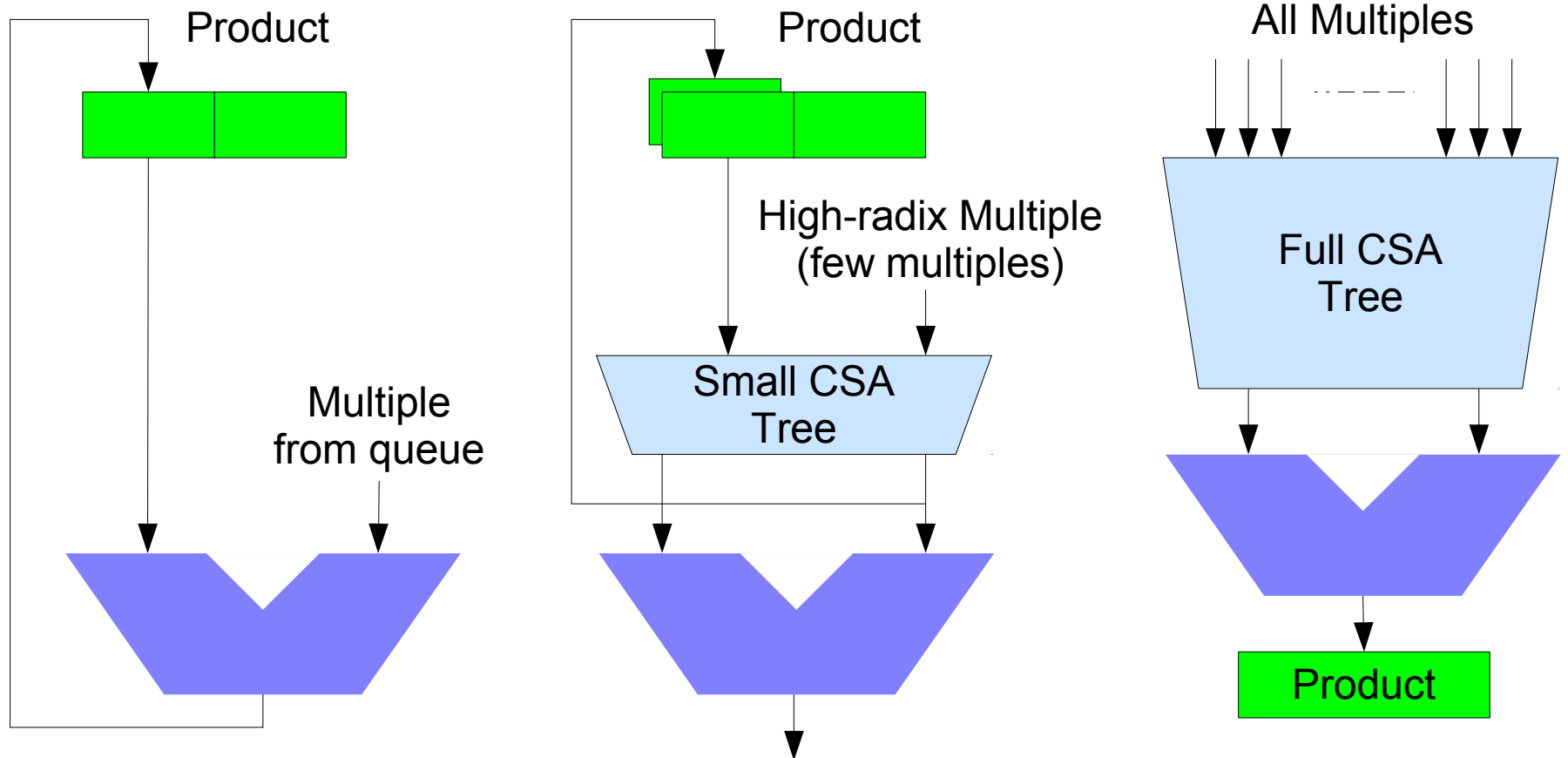




Full Tree Multipliers

- All multiples provided at the same time
- Generation logic for high-radix multiples
- Reduction tree with CSA (or RCA)
- Final CPA (for part of product only)
- Irregular (Wallace & Dadda trees) or regular configurations
- Best performance: $\Theta(\log k)$
- Highest cost (size)
- Suitable for pipeline processing


General Structure

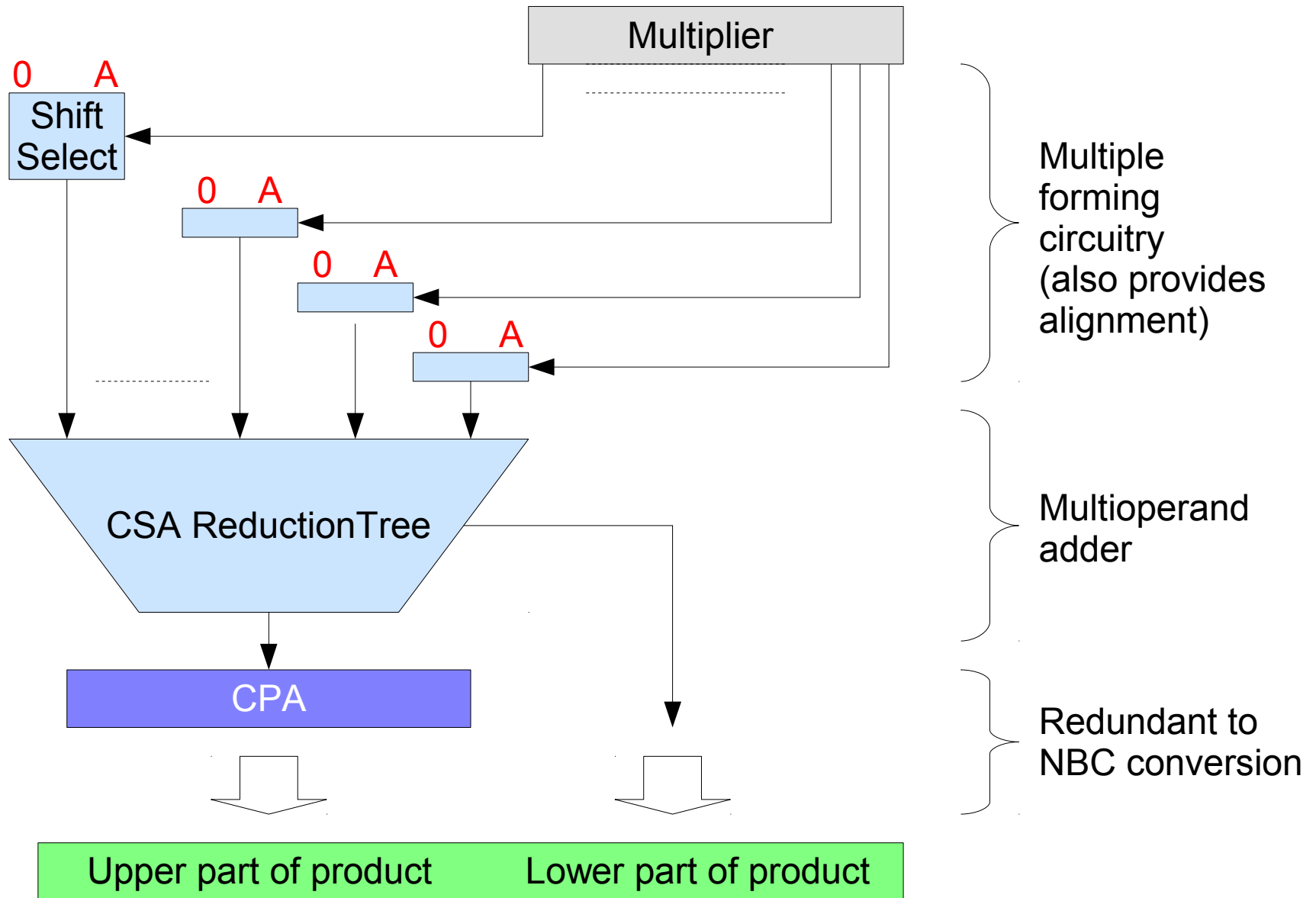

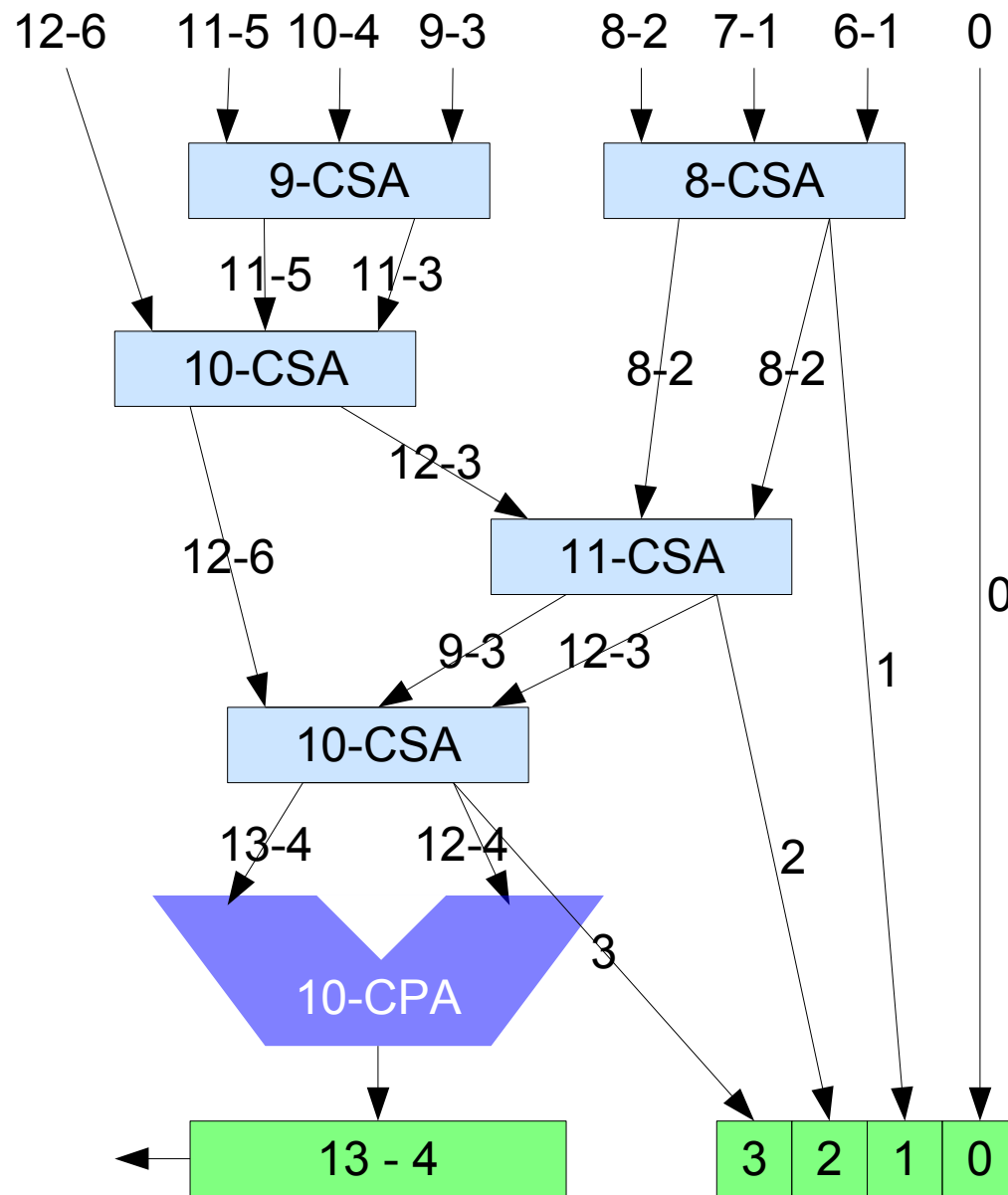Example – 7x7 CSA Tree



- Irregular reduction tree
- Variable-size CSA's
- Multiples by alignment of operands
- Lower bits of product available directly
- CPA only for upper part of product

Numbers indicate bit-positions of multiples, partial results and product



Regular Reduction Trees


- Recursive structure
- Scalable layout

  

Multiple generation logic must provide proper operands for each block


Multiplication of Long Numbers

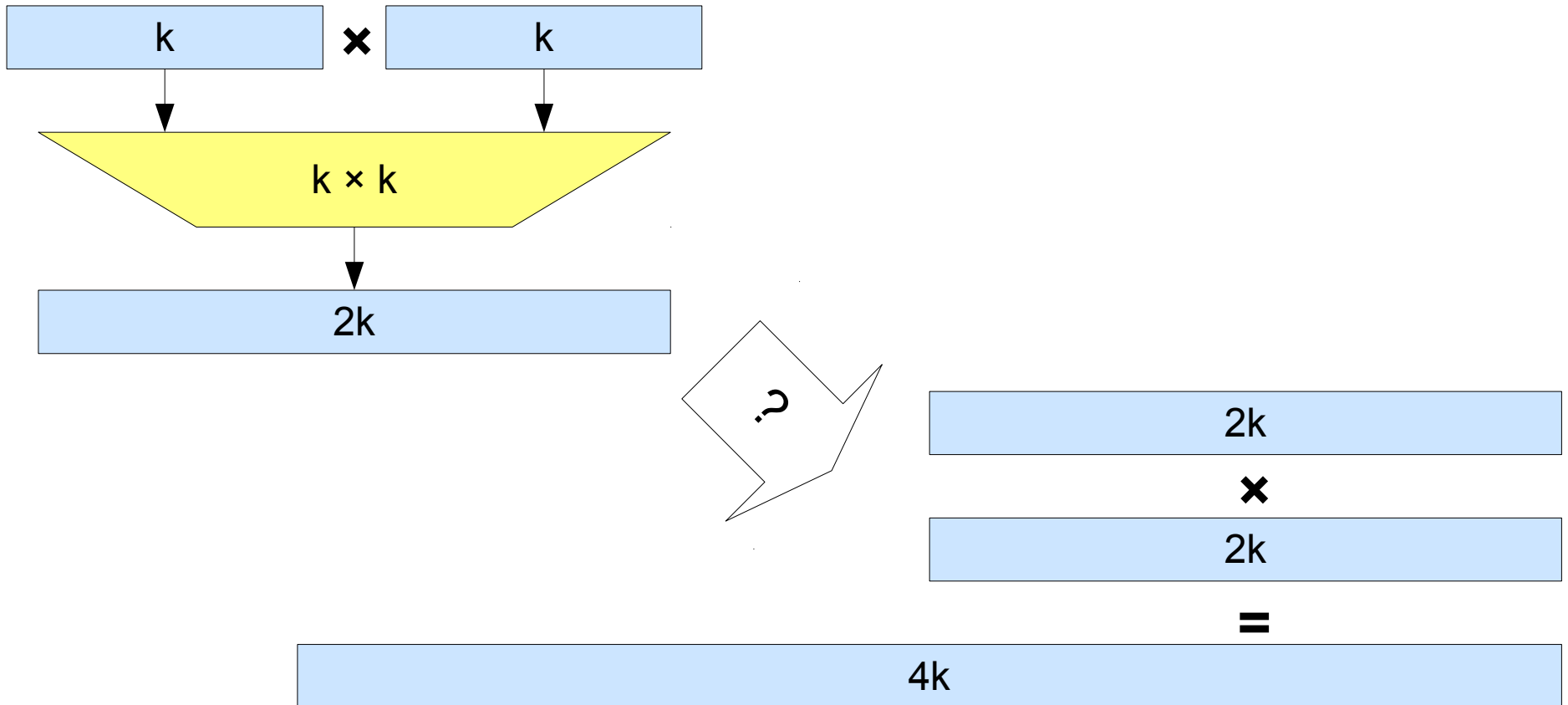- How to multiply long numbers with shorter multiplication units?
- e.g. $2k \times 2k$ numbers with k -bit multiplier?




Divide & Conquer

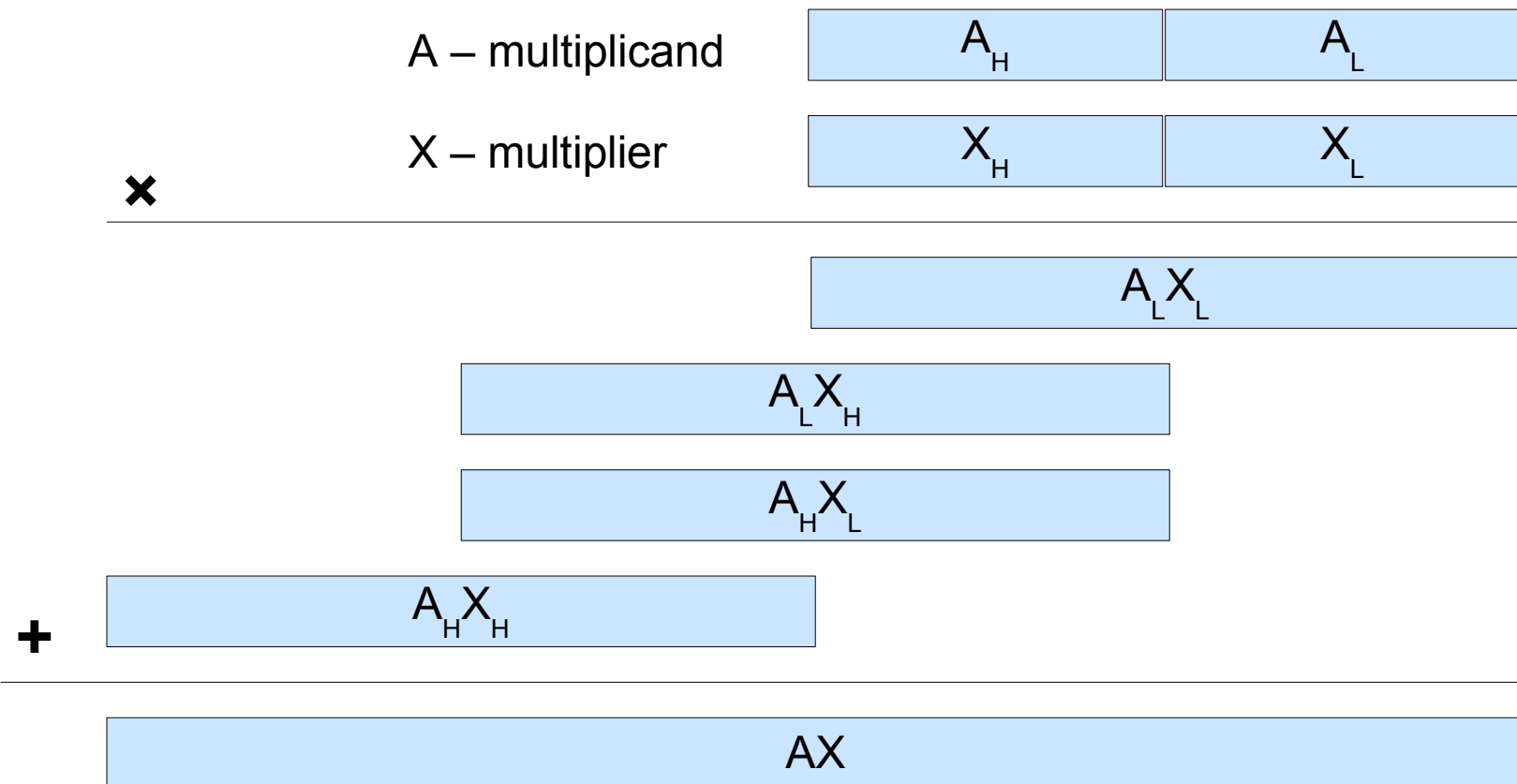- Split number into smaller parts ($2k \rightarrow 2 \times k$)
- Compute partial products ($4 \times 2k$)
- Add the partial products ($\sum 4 \times 4k$)




Divide & Conquer

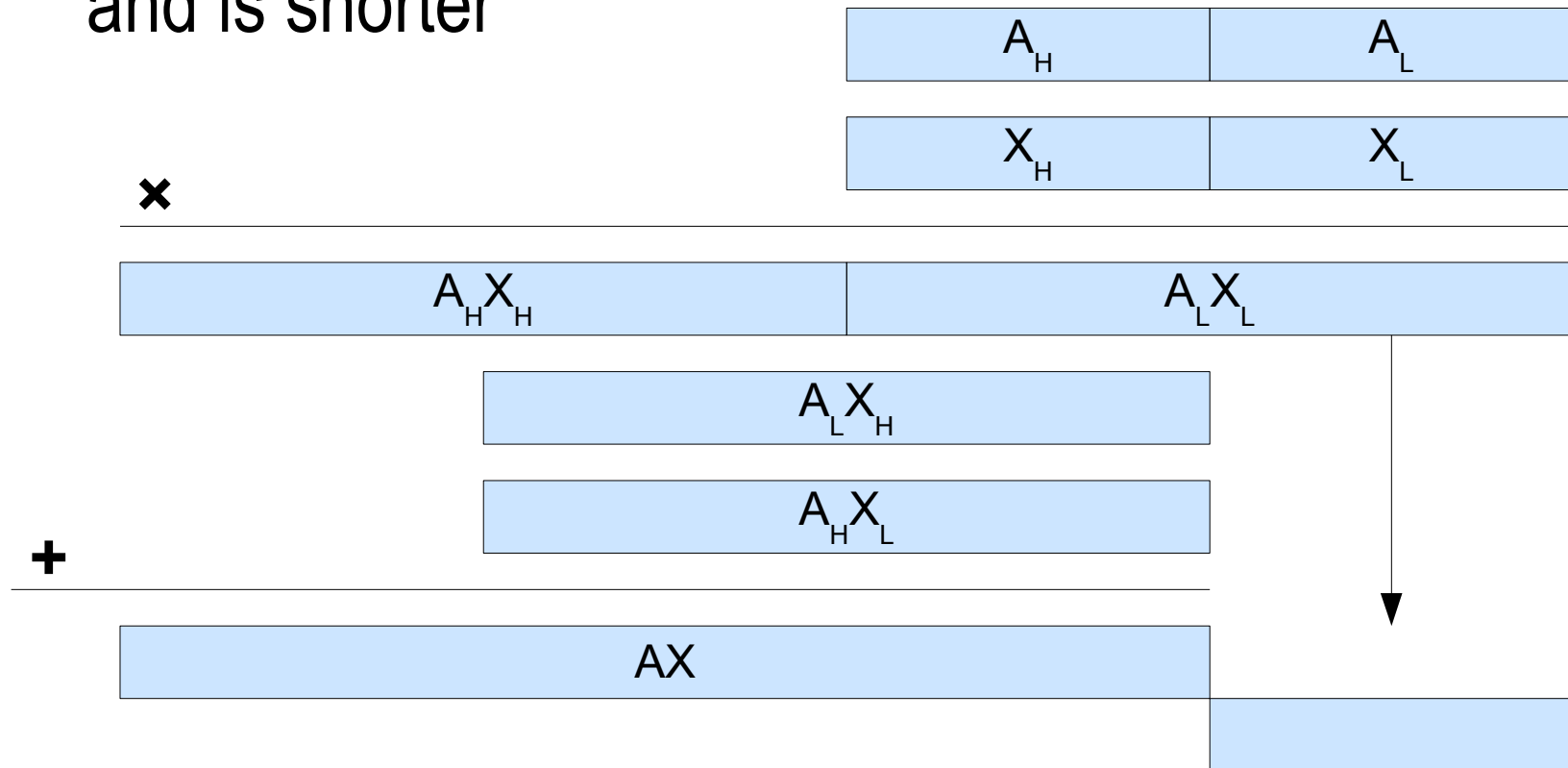- Least significant part of product is obtained directly
- There are non-overlapping partial products
- Final addition requires less partial products and is shorter




2k x 2k Divide & Conquer

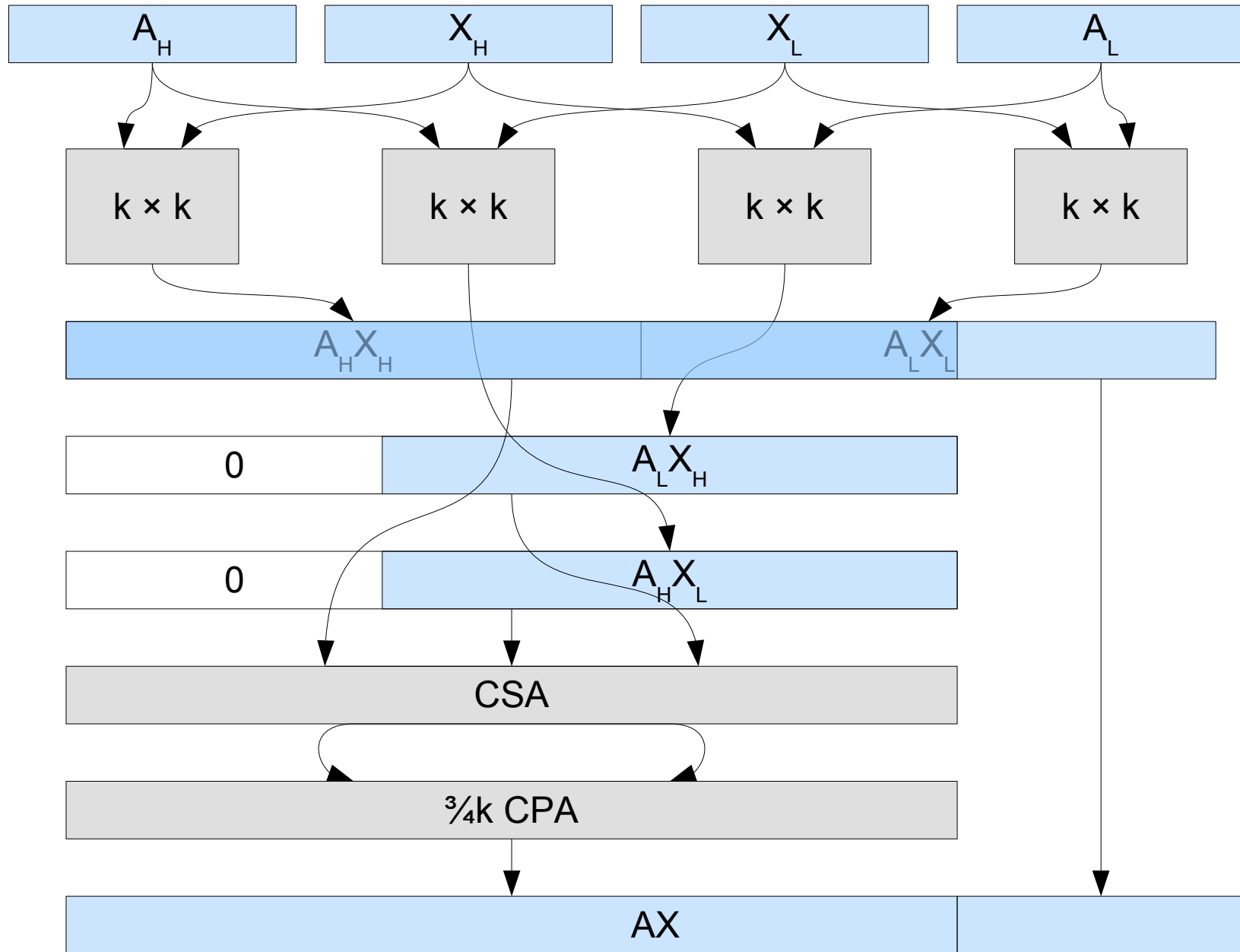

General Divide & Conquer

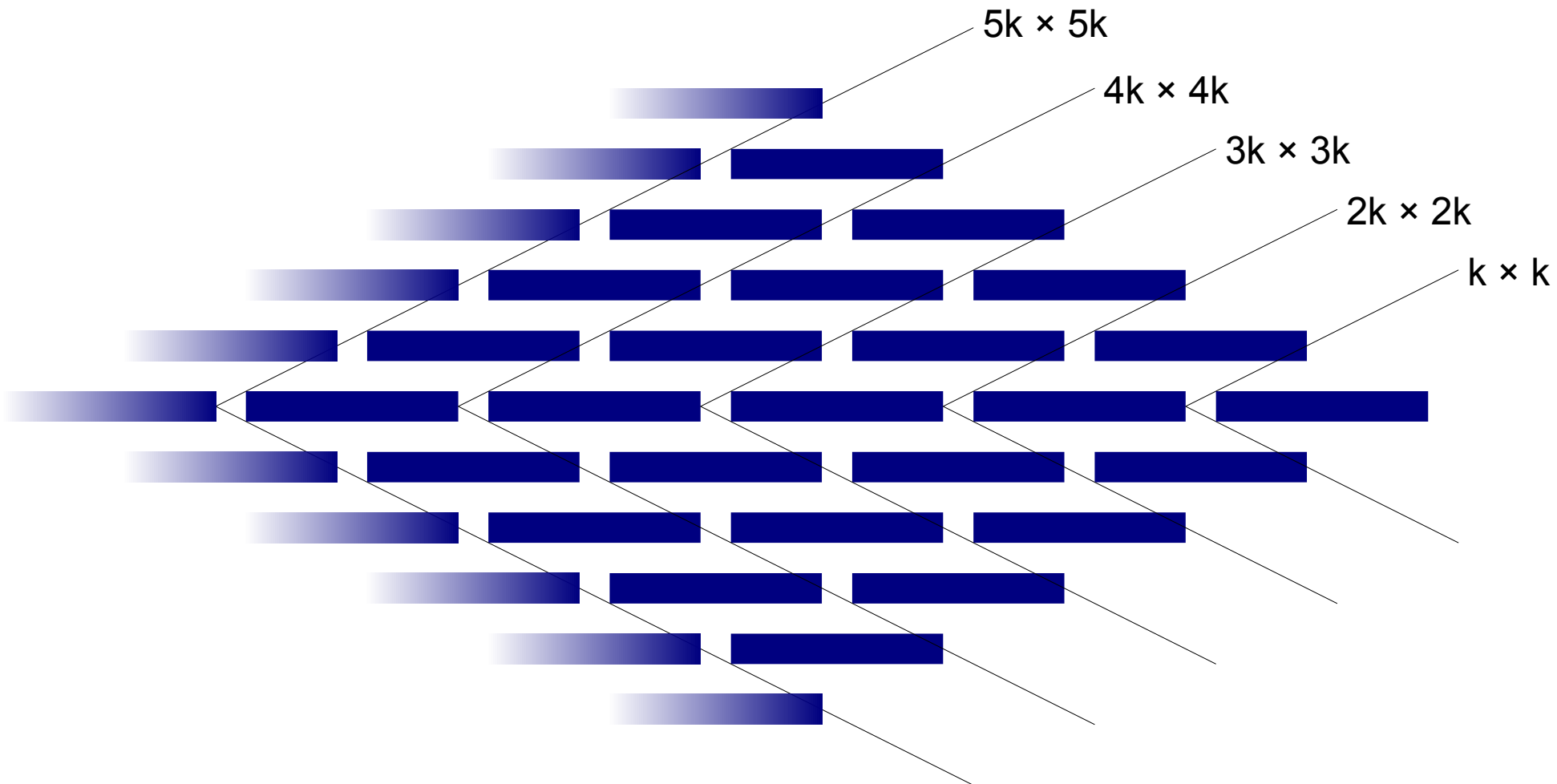- Multiplication of two $n \times k$ -bit numbers with k -bit multipliers produces $n \times n$ partial products



General Divide & Conquer

